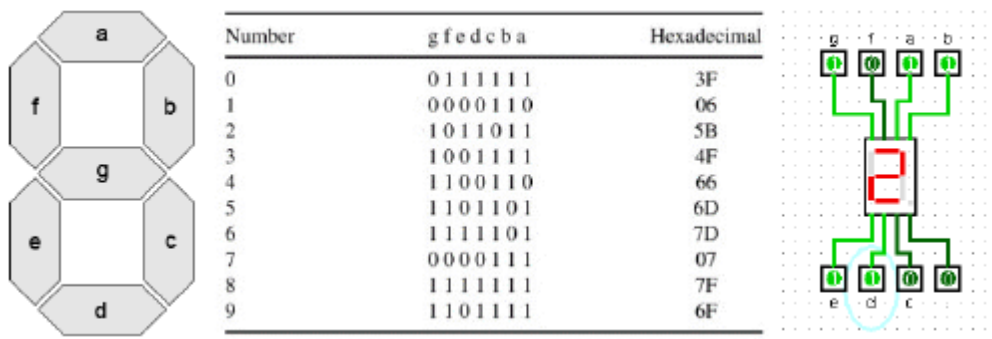


BIM203 LOGIC DESIGN HOMEWORK 2

Design a circuit that performs $F(N)=N+1$ operation for 3-bit inputs (N) and display the result on a seven-segment display (shown below). The system should accept inputs between decimal 0 and 8. Then, implement your design in Logisim;

- using only primitive gates
- using only NAND gates and necessary inverters
- using the multiplexer approach (refer to Combinational Functions slides – Multiplexer approach 1)



NOTES

- Archive the design files (truth table, optimization steps with K-maps, etc.) and Logisim files and submit via MERGEN
- Each group should make a single submission. The group members must be the same as the previous submissions.
- Indicate IDs and names of group members within the archive file.