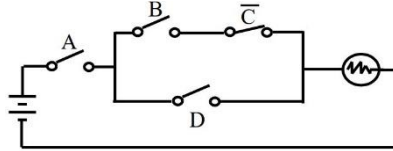


BIM203 LOGIC DESIGN - HOMEWORK 1

1) Do the following conversions/codings:

- a) Convert 1101.40625_{10} to binary c) Convert 723_8 to hexadecimal
b) Convert 999_{10} to octal d) Encode 2022_{10} using BCD



2) Light is on ($L = 1$) for $L (A, B, C, D)$ and off ($L = 0$), otherwise. Considering the above electronic circuit;

- a) Draw the truth table and logic diagram.
b) Compute the costs L , G , and GN .

3) Prove the identity of each of the following Boolean equations using algebraic manipulations. Please also specify which theorems you used.

- a) $A'B' + A'B + AB' = A' + B'$ b) $X'Y + Y'Z' + XY + Y'Z = 1$
c) $X + XY + X'Z + YZ' = X + Y + Z$ d) $A'B + AC' + ABC = B + AC'$

4)

$$G(A, B, C, D) = \sum m(1, 4, 6, 7, 8, 9, 12, 13, 14, 15) \quad G(A, B, C, D) = \sum m(0, 2, 4, 5, 6, 10, 13) + \sum d(1, 7, 8)$$

For each binary expression above;

- a) Find the simplest expression using K-map.
b) Draw the simplified circuit in Logisim.

NOTES

- Each group (consisting of max. 2 students) should make single submission.
- Indicate IDs and names of the group members within the report.
- You cannot change your group in the upcoming assignments.
- For your report, you can use a text processor software like MS Word.
- Submit your work before the deadline.