

---

# **BIM203 Logic Design**

---

**Implementation Technology and Logic Design**

# Overview


---

- **Design Procedure**
  - 1. Specification**
  - 2. Formulation**
  - 3. Optimization**
  - 4. Technology Mapping**
  - 5. Verification**
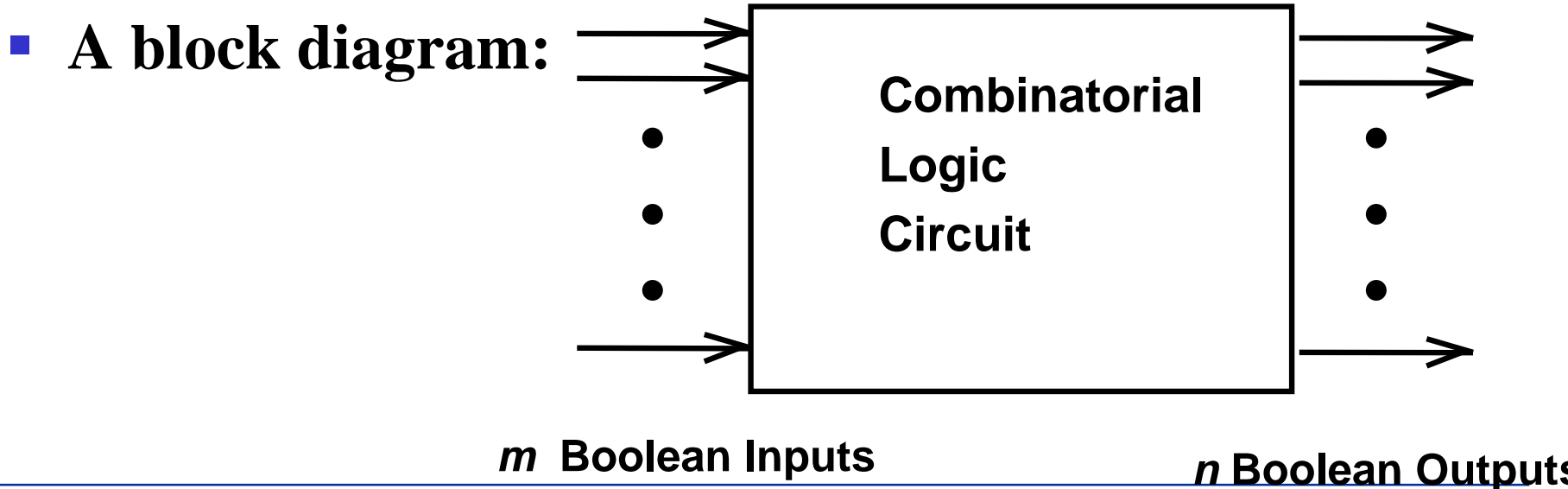
# Combinational Circuits

---

- A combinational logic circuit has:
  - A set of  $m$  Boolean inputs,
  - A set of  $n$  Boolean outputs, and
  - $n$  switching functions, each mapping the  $2^m$  input combinations to an output such that the current output depends only on the current input values



# Design Procedure

---

## 1. Specification

- Write a specification for the circuit if one is not already available

## 2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- Apply hierarchical design if appropriate

## 3. Optimization

- Apply optimization i.e., employ K-maps
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

# Design Procedure

---

## 4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected

## 5. Verification

- Verify the correctness of the final design manually or using simulation

# Design Example

---

## 1. Specification

- **BCD to Excess-3 code converter**
- **Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits**
- **BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively**
- **Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word**
- **Implementation:**
  - **multiple-level circuit**
  - **NAND gates (including inverters)**

# Design Example (continued)

## 2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables

- BCD:

A,B,C,D

- Variables

- Excess-3

W,X,Y,Z

- Don't Cares

- BCD 1010

to 1111

Input BCD	Output Excess-3
A B C D	W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1

# Design Example (continued)





## 3. Optimization

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$


$$Z = \bar{D}$$

 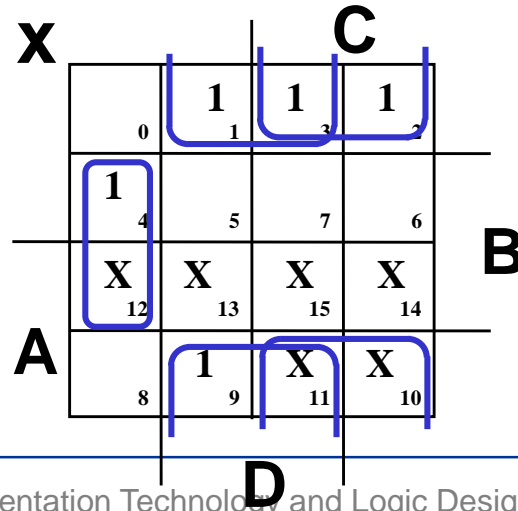  



# Design Example (continued)

## 4. Technology Mapping

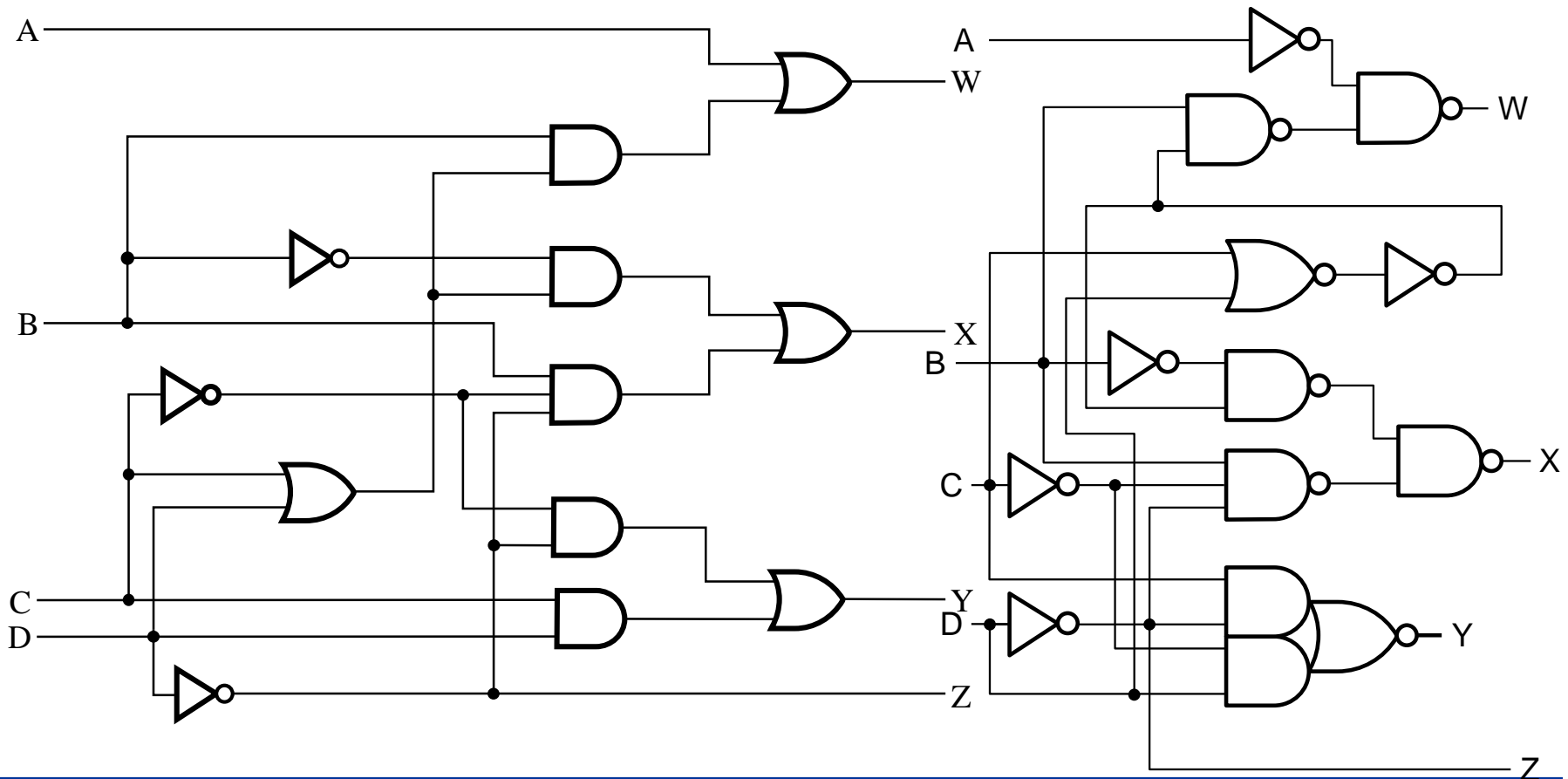

# Technology Mapping

---

- **Mapping Procedures**
  - **To NAND gates**
  - **To NOR gates**
  - **Mapping to multiple types of logic blocks in covered in the reading supplement:  
Advanced Technology Mapping.**

# Mapping to NAND gates

---

## ■ Assumptions:


- Gate loading and delay are ignored
- Cell library contains an inverter and  $n$ -input NAND gates,  $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

## ■ The mapping is accomplished by:


- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs

# NAND Mapping Algorithm


- **Replace ANDs and ORs:**

 

 
- **Repeat the following pair of actions until there is at most one inverter between :**
  - a.** A circuit input or driving NAND gate output, and
  - b.** The attached NAND gate inputs.




# NAND Mapping Example

 


(a)

 

(b)

 

(c)

 

(d)

# Mapping to NOR gates

---

- **Assumptions:**


- Gate loading and delay are ignored
- Cell library contains an inverter and  $n$ -input NOR gates,  $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

- **The mapping is accomplished by:**


- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs

# NOR Mapping Algorithm


- Replace ANDs and ORs:

 

 - Repeat the following pair of actions until there is at most one inverter between :
  - a. A circuit input or driving NAND gate output, and
  - b. The attached NAND gate inputs.



# NOR Mapping Example

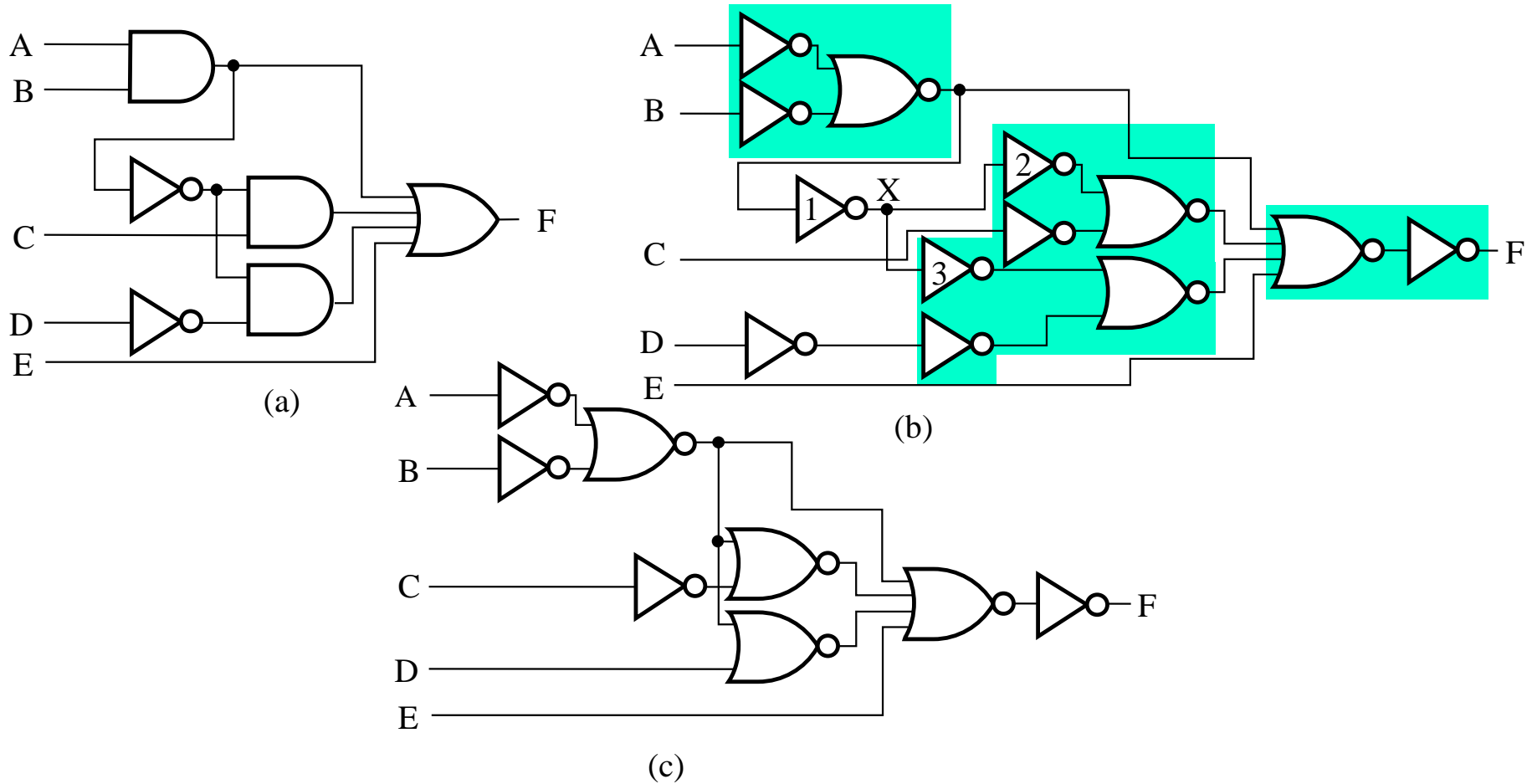



# Verification

---

**5. Verification :** show that the final circuit designed implements the original specification

- **Simple specifications are:**
  - truth tables
  - Boolean equations
  - HDL (Hardware Descriptor Language) code
- **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**

# Basic Verification Methods

---

## ■ Manual Logic Analysis

- Find the truth table or Boolean equations for the final circuit
- Compare the final circuit truth table with the specified truth table, or
- Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

## ■ Simulation

- Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification

# Verification Example: Manual Analysis

---

- **BCD-to-Excess 3 Code Converter**
  - Find the SOP Boolean equations from the final circuit.
  - Find the truth table from these equations
  - Compare to the formulation truth table
- **Finding the Boolean Equations:**

$$T_1 = \overline{\overline{C} + \overline{D}} = C + D$$

$$W = \overline{\overline{A} (\overline{T_1} \overline{B})} = A + B T_1$$

$$X = (T_1 B) (B \overline{C} \overline{D}) = \overline{B} T_1 + B \overline{C} \overline{D}$$

$$Y = \overline{\overline{C} \overline{D} + \overline{C} D} = CD + \overline{C} \overline{D}$$

# Verification Example: Manual Analysis

- Find the circuit truth table from the equations and compare to specification truth table:

Input BCD A B C D	Output Excess-3 WXYZ
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1

**The tables match!**


# Verification Example: Simulation

---

- **Simulation procedure:**
  - **Use a schematic editor or text editor to enter a gate level representation of the final circuit**
  - **Use a waveform editor or text editor to enter a test consisting of a sequence of input combinations to be applied to the circuit**
    - **This test should guarantee the correctness of the circuit if the simulated responses to it are correct**
    - **Short of applying all possible “care” input combinations, generation of such a test can be difficult**

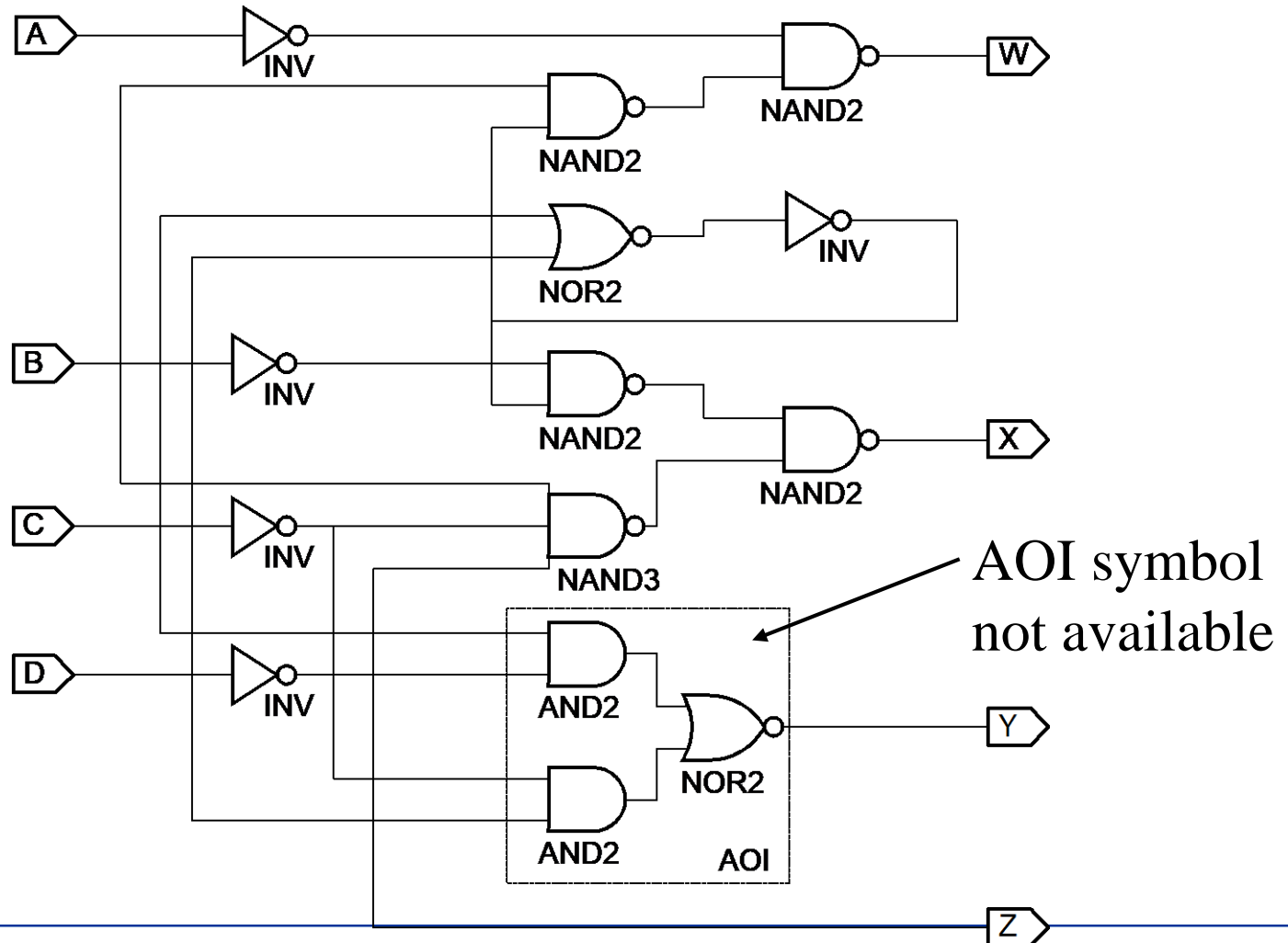
# Verification Example: Simulation

- Enter BCD-to-Excess-3 Code Converter Circuit Schematic


 
# Verification Example: Simulation


- Enter waveform that applies all possible input combinations:



- Are all BCD input combinations present? (Low is a 0 and high is a one)
 
# Verification Example: Simulation

- Run the simulation of the circuit for 120 ns



- Do the simulation output combinations match the original truth table?



# Terms of Use

---

- **All (or portions) of this material © 2008 by Pearson Education, Inc.**
- **Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.**
- **These materials or adaptations thereof are not to be sold or otherwise offered for consideration.**
- **This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.**