
BIM203 Logic Design

Sequential Circuit Design Example

Specification

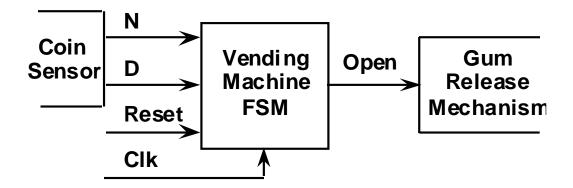- deliver package of gum after 15 cents deposited
- single coin slot for dimes (10 cents), nickels (5 cents)
- no change





Inputs: N, D, reset

Output: open

Coin Possibilities

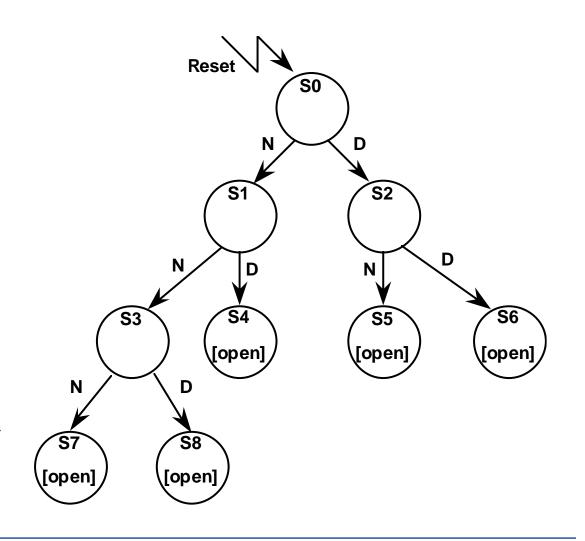- three nickels
- nickel, dime
- dime, nickel
- two dimes
- two nickels, dime



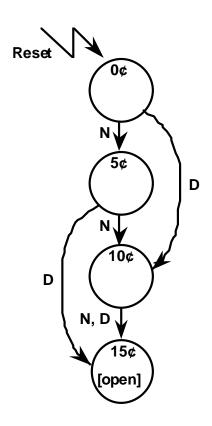


Present State	Inputs D N		Next State	Output Open
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	X	Χ
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	X	Χ
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	Χ	X
15¢	Χ	Χ	15¢	1

reuse states whenever possible

Symbolic State Table

State Encoding

Present State Q_1 Q_0	Input D	ts N	Next S D ₁	tate D ₀	Output Open
0 0	0	0	0	0	0
	0	1	0	1	0
	1	0	1	0	0
	1	1	X	Χ	X
0 1	0	0	0	1	0
	0	1	1	0	0
	1	0	1	1	0
	1	1	X	X	X
1 0	0	0	1	0	0
	0	1	1	1	0
	1	0	1	1	0
	1	1	X	X	X
1 1	0	0	1	1	1
	0	1	1	1	1
	1	0	1	1	1
	1	1	X	Χ	X
		I			

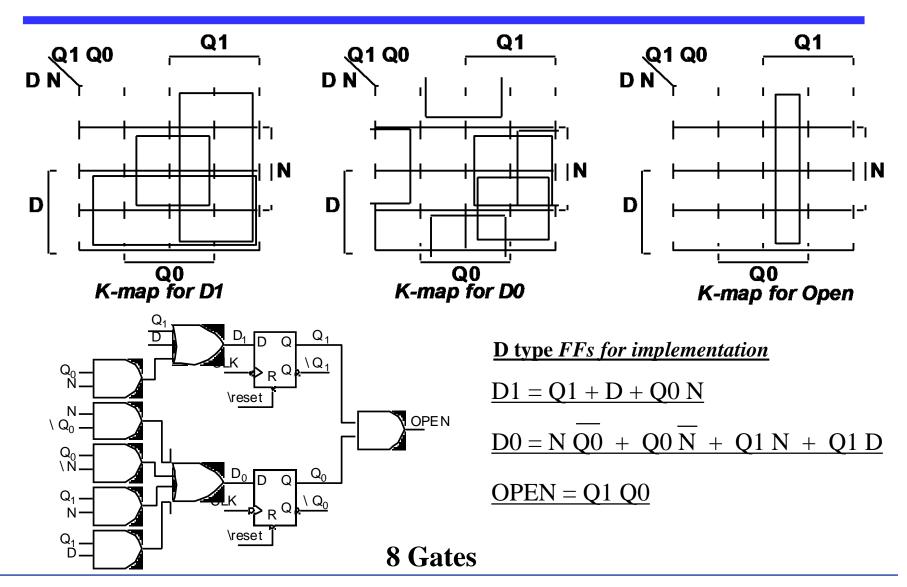

Terms of Use

- All (or portions) of this material © 2008 by Pearson Education, Inc.
- Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.
- These materials or adaptations thereof are not to be sold or otherwise offered for consideration.
- This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.