

Soru 1

$$a = 10 \angle -30^\circ, b = 12 \angle -30^\circ$$

Time Domain

a isin

$$j\omega c = j \cdot 377 \cdot 10^{-6} = 3,22 \cdot 10^{-4} j + 0$$

$$j\omega c = 3,22 \cdot 10^{-4} \angle 90^\circ$$

$$I_c = (3,22 \cdot 10^{-4} \angle 90^\circ) \times (10 \angle -30^\circ)$$

$$= (0 + 3,22 \cdot 10^{-4} j) \times 10 (\cos -30^\circ + j \sin -30^\circ)$$

\sim
8,6 - 5j

$$= 3,2422 \cdot 10^{-3} + 1,885 \cdot 10^{-3}$$

$$I_c = 3,75 \cdot 10^{-3} \angle 59,82^\circ$$

b isin

$$I_c = (3,22 \cdot 10^{-4} \angle 90^\circ) \times (12 \angle -30^\circ)$$

$$= 3,22 \cdot 10^{-4} j \times (10,32 - 5j)$$

$$\approx 3,890 \cdot 10^{-3} j + 2,262 \cdot 10^{-3}$$

$$\approx 4,499 \cdot 10^{-3} \angle 59,82^\circ$$

$$I_c \approx 4,499 \cdot 10^{-3} \angle 59,82^\circ$$

Frequency Domain

a isin

$$V = \frac{3,75 \cdot 10^{-3} \angle 59,82^\circ}{3,22 \cdot 10^{-4} \angle 90^\circ} \approx [9,94 \angle -30,18^\circ]$$

b isin


$$\frac{4,499 \cdot 10^{-3} \angle 59,82^\circ}{3,22 \cdot 10^{-4} \angle 90^\circ} \approx [11,93 \angle -30,18^\circ]$$

8.5 Calculate the current in the capacitor shown in Fig. P8.5 if the voltage input is

(a) $v_1(t) = 10 \cos(377t - 30^\circ)$ V.

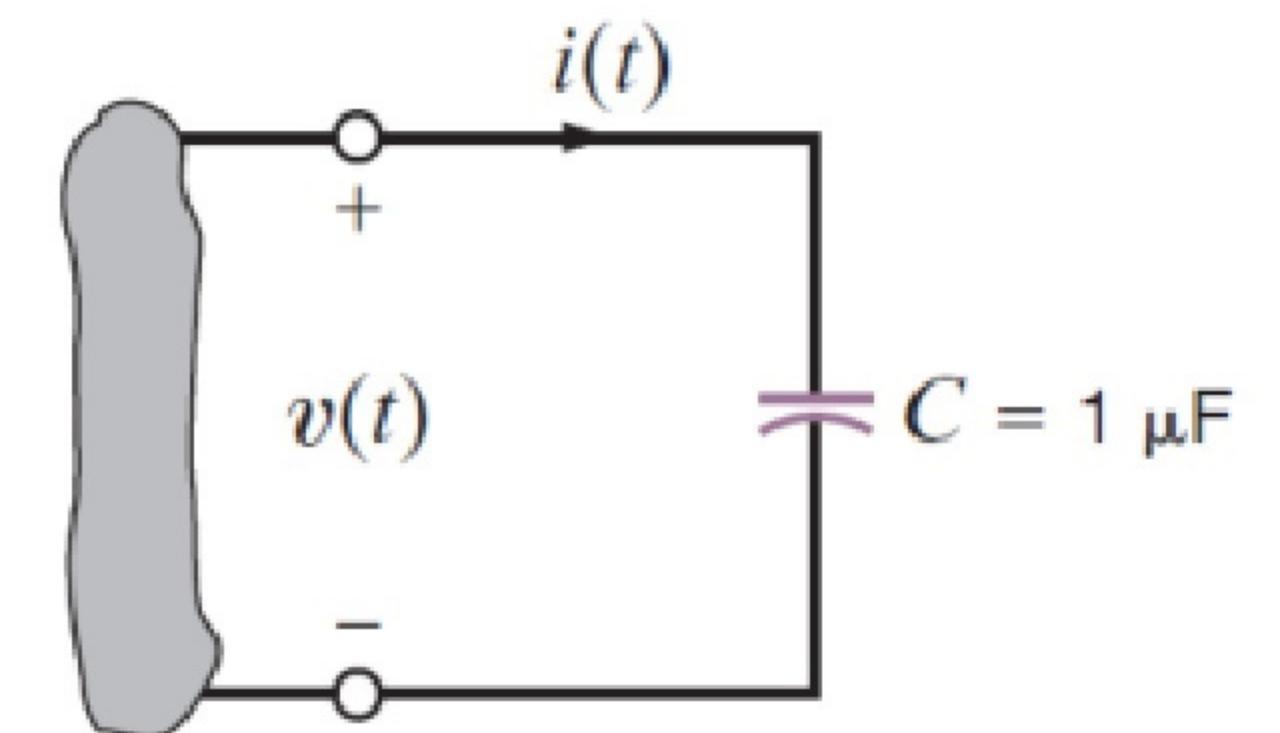(b) $v_2(t) = 12 \sin(377t + 60^\circ)$ V.

Give the answers in both the time and frequency domains.



8.7

$$\underline{Z_L} = (2\pi \cdot 60) (10^{-2}) j \\ \approx 2,769 j$$

$$\underline{Z_C} = \frac{-j}{w.c} = \frac{-j}{(2\pi \times 60) (10^{-5})} \\ \underline{Z_C} \approx -265,2 j$$

$$\underline{Z_{eq}} = \underline{Z_L} + (1 \parallel (2 + \underline{Z_C}))$$

$$= 3,269 \angle 90^\circ + \frac{2 - 265,2}{3 - 265,2j} \rightarrow \frac{265,2 \angle -89,56^\circ}{265,2 \angle -89,35^\circ} \angle 110,21^\circ$$


$$= 3,269 \angle 90^\circ + 110,21^\circ$$

$$= 3,269 j + 0,999 + 3.664 \times 10^{-3} j$$


$$\underline{Z_{eq}} = [0.999 + 3.722 j]$$

$$Z = [3.90 \angle 25^\circ]$$

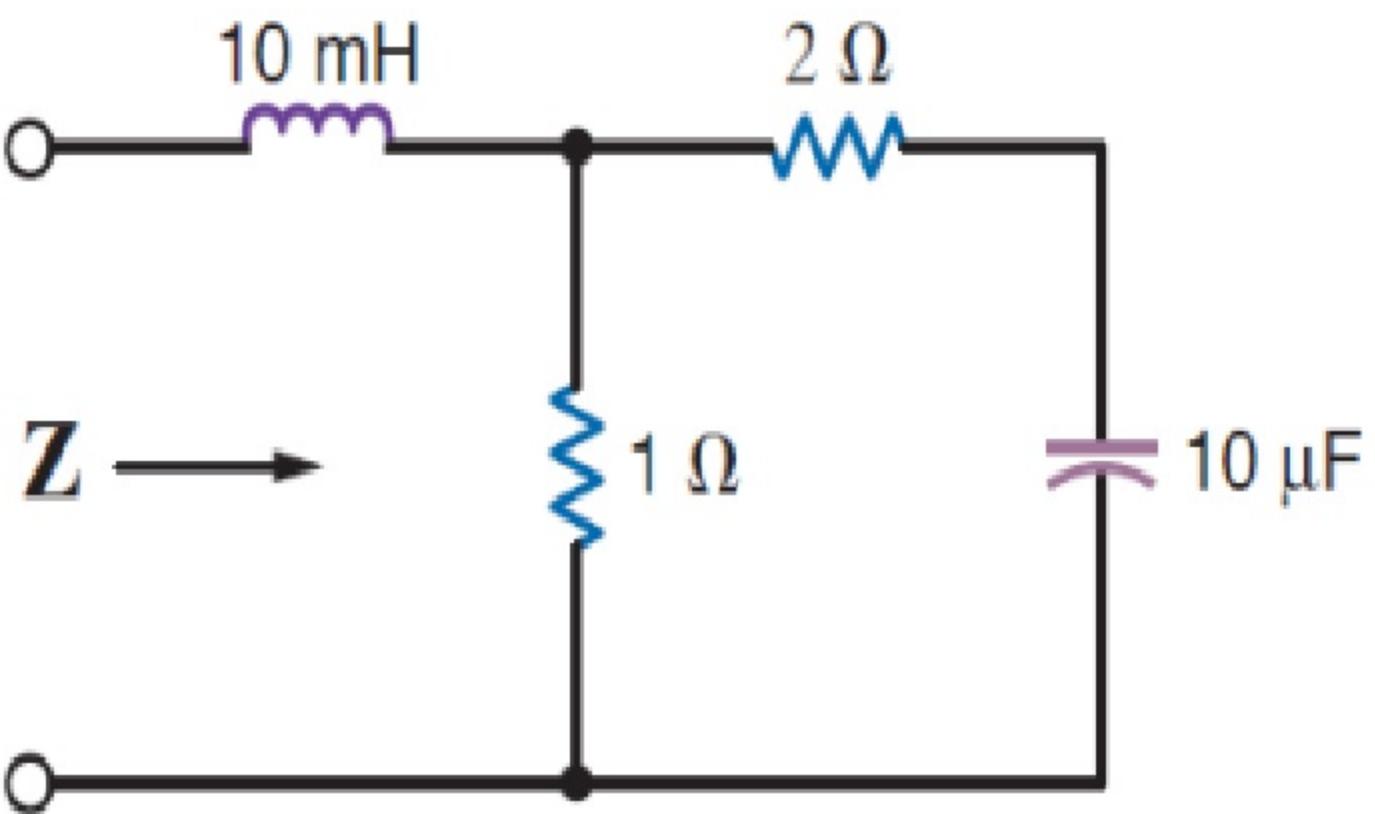8.7 Find the impedance, Z , shown in Fig. P8.7 at a frequency of 60 Hz.



8.9

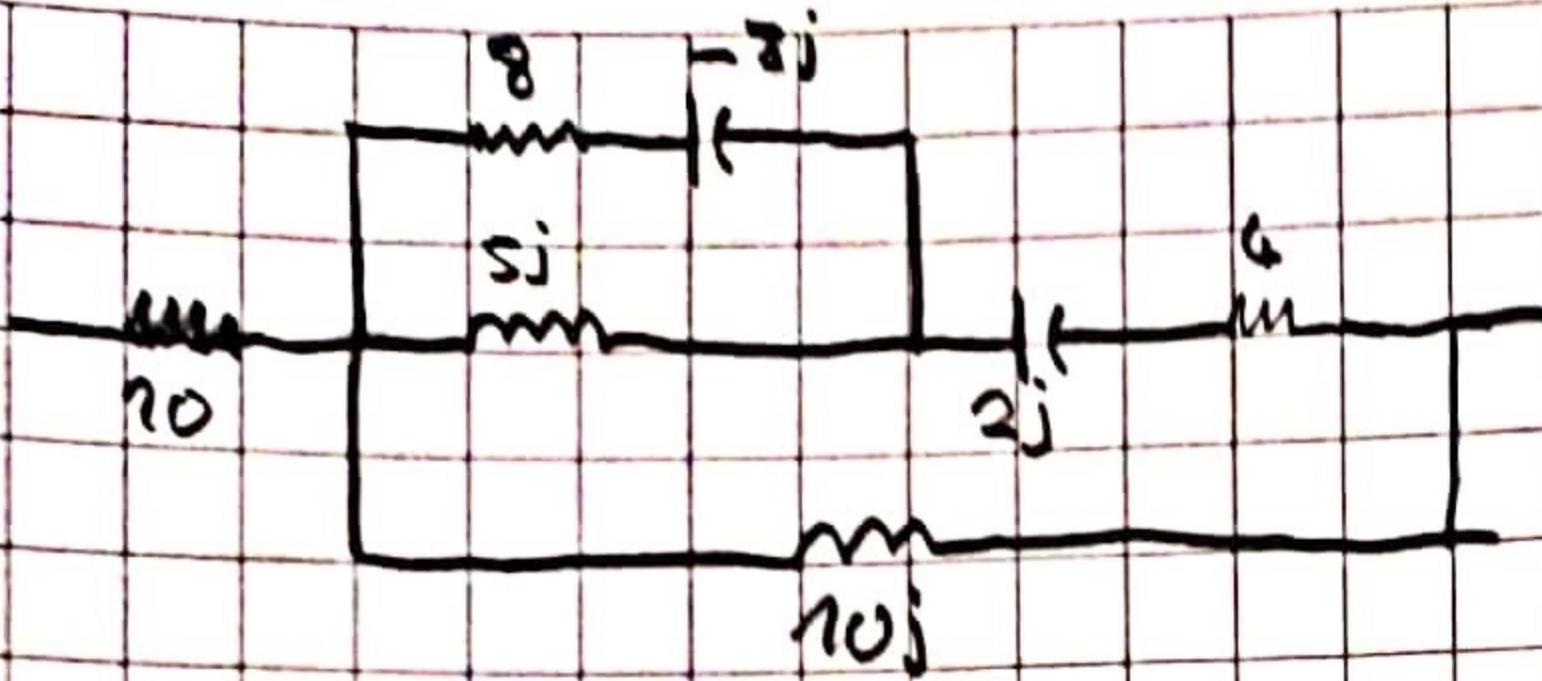

içeriği氯zenleyelim

$$\frac{40j + 40}{8-3j} + 4-2j = 2,34 + 6,02j + 4-2j = 6,74 + 4,02j$$

Yen. hali:


$$10 + \left(\frac{(6,74 + 4,02j) \cdot 10j}{6,74 + 14,02j} \right)$$

$$10 + \left(\frac{67,4j - 40,2}{6,74 + 14,02j} \right) = 12,78 + 4,206j$$

$$Z_{eq} = 12,78 + 4,206j$$

$$Z = 13.45 \angle 18.02^\circ$$

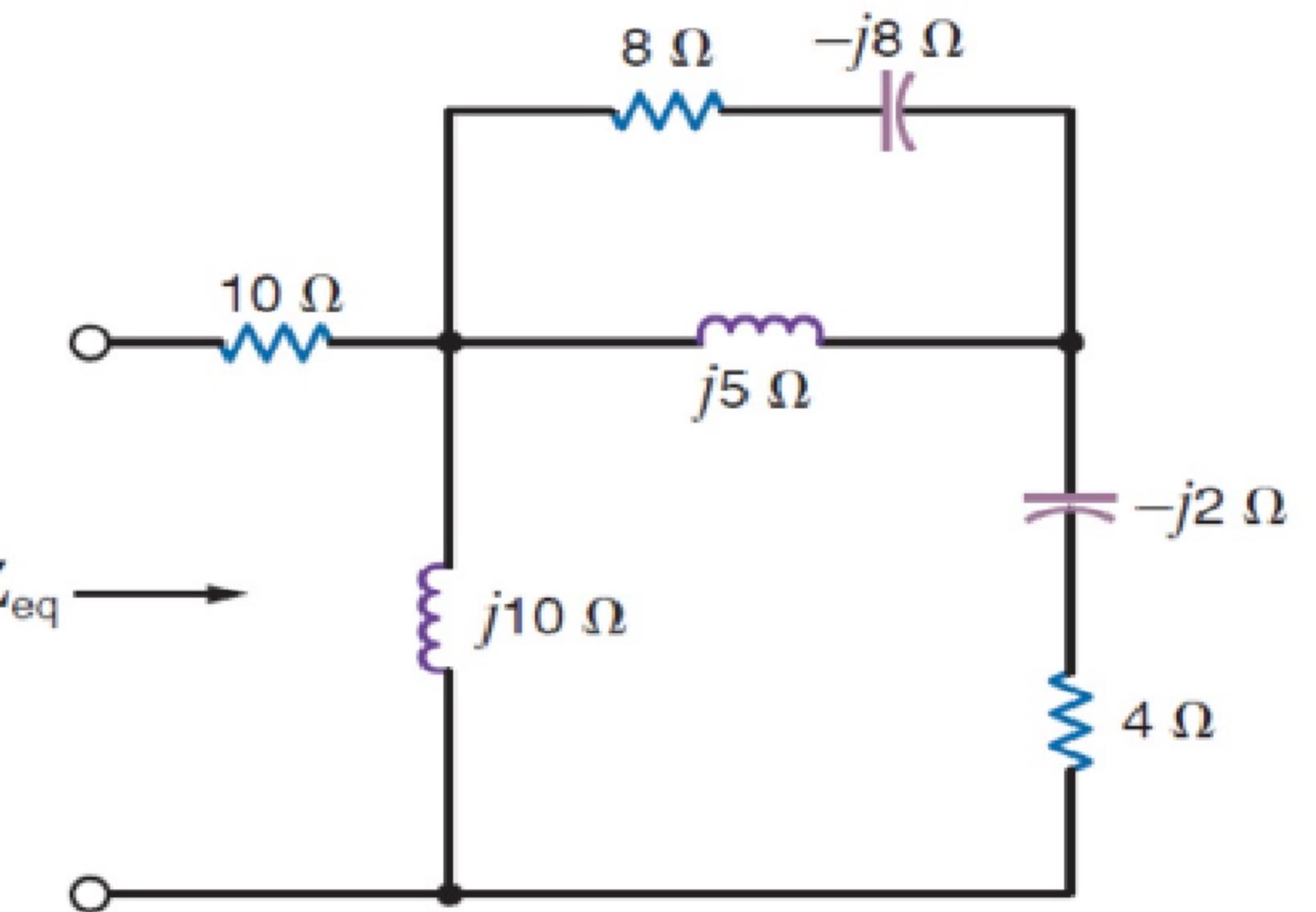8.9 Find the equivalent impedance for the circuit in Fig. P8.9.



8.13

$$Z_L = (2\pi \cdot 60) \times (10^{-2})$$

$$Z_L \approx 3.769j$$

$$Z_C = \frac{-j}{(2\pi \cdot 60)(5 \cdot 10^{-4})}$$

$$Z_C \approx -5.308j$$


$$Z_{eq} = 2 + (3.769j \parallel (4 - 5.308j))$$

$$\frac{2 + 3.769j \times (4 - 5.308j)}{4 - 1.536j} = \frac{15.026j + 19.994}{4 - 1.536j} + 2$$


$$Z_{eq} = 5.09 + 4.98j$$

$$Z_{eq} = 7.1 \angle 44.2^\circ$$

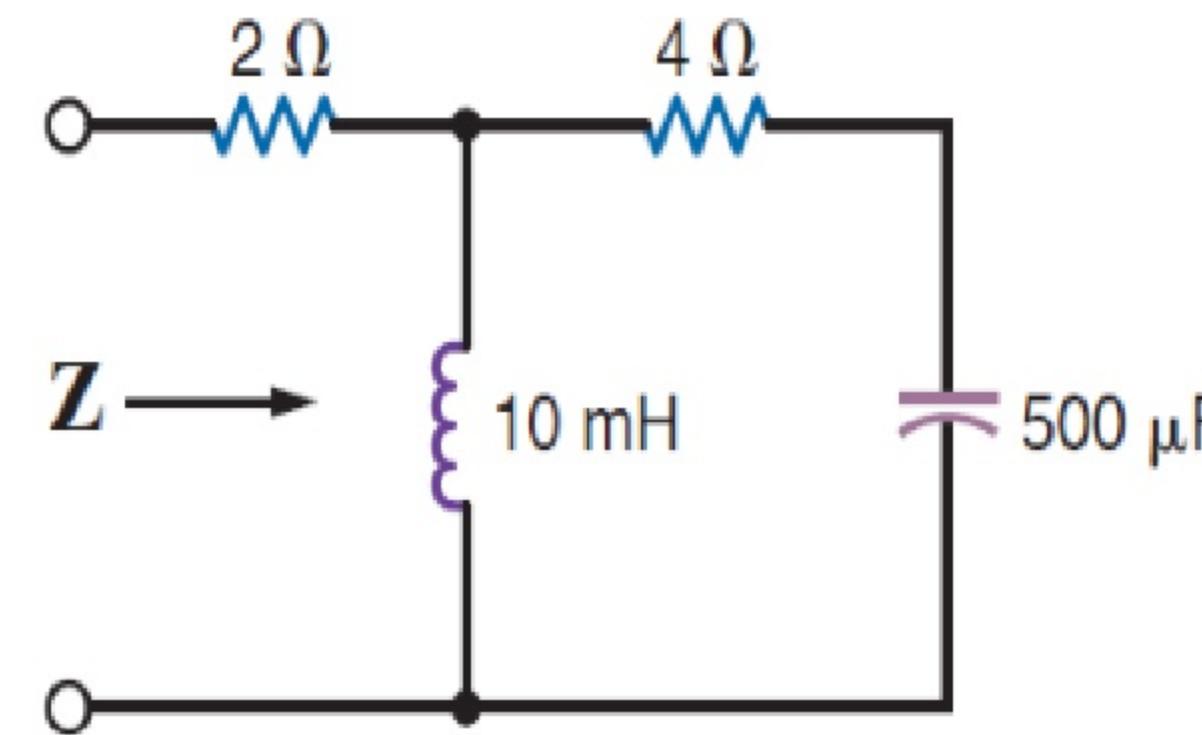8.13 Find the impedance, Z, shown in Fig. P8.13 at a frequency of 60 Hz.



Q.15

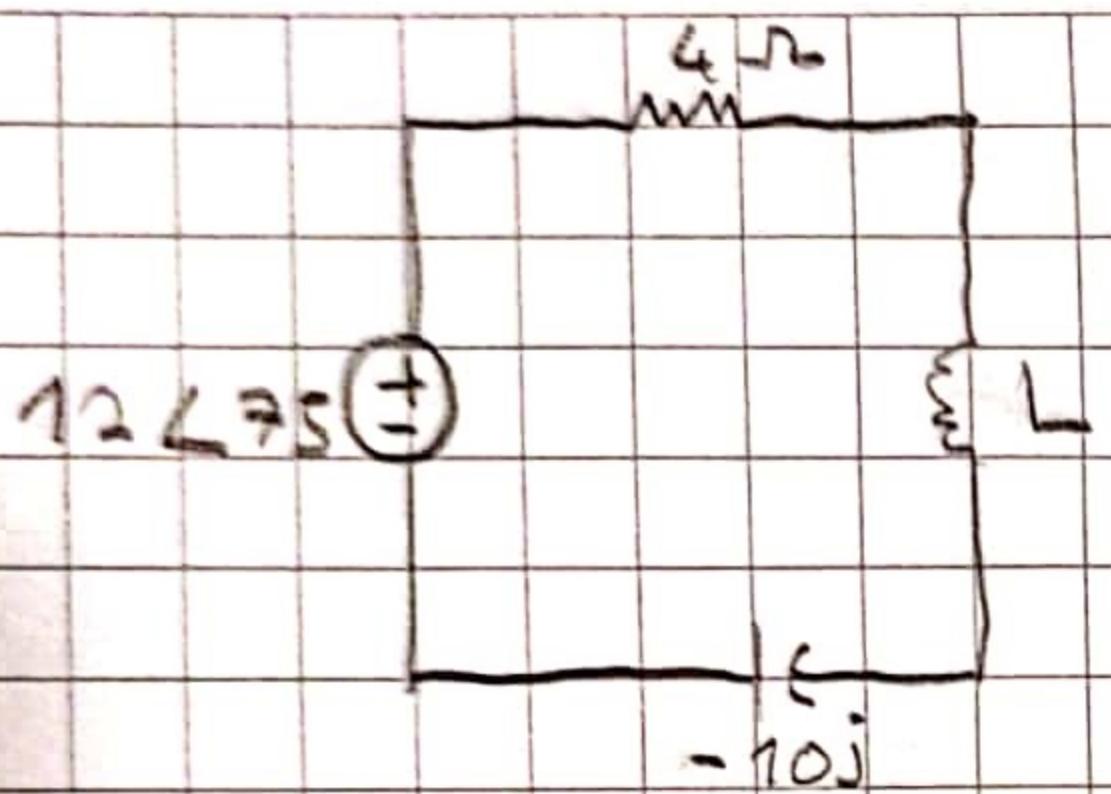

$$12 \cos(1000t + 75^\circ) V$$

$$R_C = \frac{-j}{100 \cdot 10^{-6} \cdot 1000j}$$

$$Z = R + jX = 10j$$

$$Z = R \text{ ohm in series}$$


$$1000 \cdot L \cdot j = +10j$$

$$L = 10^{-2}$$

impedance
 $Z = R$

$L = 10 \text{ mH}$

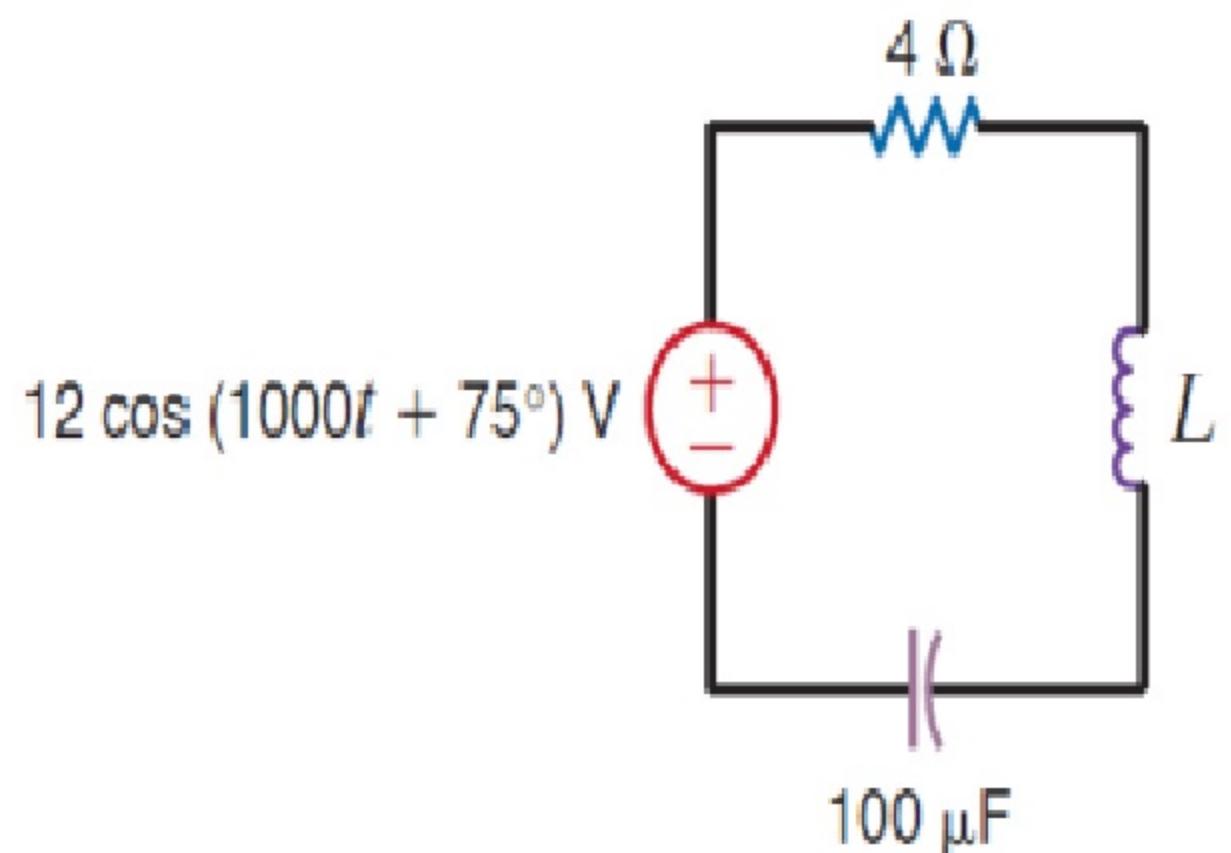8.15 In the circuit shown in Fig. P8.15, determine the value of the inductance such that the current is in phase with the source voltage.



8.25

$$v(t) = 5 \cos 500t \text{ V}$$

$$v = 5 \angle 0^\circ$$

$$i(t) = 0,4 \cos(500t - 30^\circ) \text{ A}$$

$$I = 0,4 \angle -30^\circ$$

$$Z_{eq} = \frac{v}{I} = \frac{5 \angle 0^\circ}{0,4 \angle -30^\circ} = 12,5 \angle 30^\circ$$

$$Z_{eq} = 12,5 \angle 30^\circ, 12,5 (\cos 30) + i 12,5 (\sin 30) = 10,82 + 6,25j$$

$$\text{ip } v(t) = 5 \cos 1000t \text{ V} \quad i(t) = ?$$

$$i(t) = \frac{V}{Z}$$

$$\frac{5}{10,82 + 2 \times (6,25j)}$$

$$I = \frac{5 \angle 0^\circ}{16L^{-49}} \quad I = 0,3125 \angle -49^\circ$$

$$i(t) = 0,3125 \cos(1000t - 49^\circ) \text{ A}$$

- 8.25** In the diagram in Fig. P8.25 when $v(t) = 5 \cos 500t \text{ V}$, $i(t) = 0,4 \cos(500t - 30^\circ)$ A. Calculate $i(t)$ if $v(t) = 5 \cos 1000t \text{ V}$.

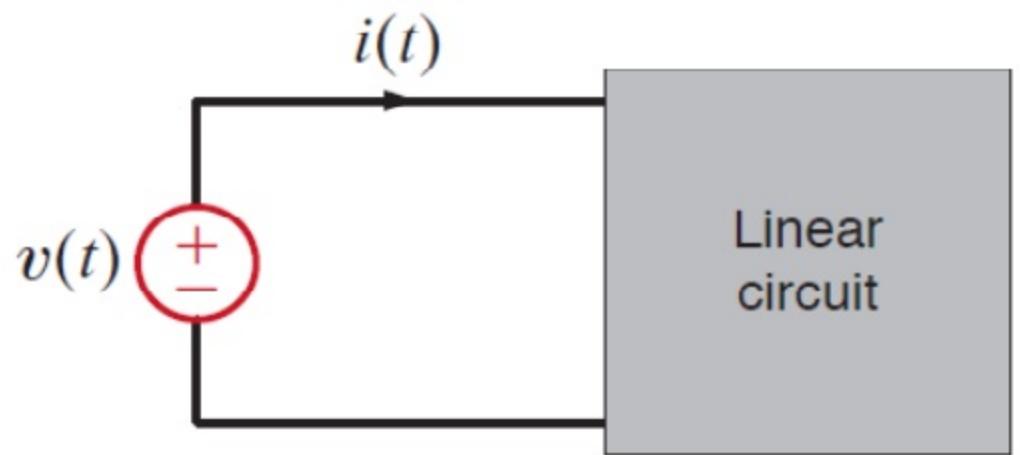


Figure P8.25

$$\omega = \frac{1000}{500 \cdot 2} = 1000$$

8.18

$$Z_L = (2\pi \cdot 400) (10^{-2}) j$$

$$\frac{Z_{eq}}{6 + Z_L + Z_C} = \frac{6Z_C + Z_L \cdot Z_C}{6 + Z_L + Z_C}$$

$$[2\pi \cdot 400 = 2512]$$

$$\frac{-6j + \frac{10^{-2}}{C}}{6 + j(10^{-2}\omega - \frac{1}{\omega C})}$$

paylaşılacak değerlerin olmamalı
için esleniştirilecektir.

amaç iki farklı katsayı 0 yapmak

$$R = Z$$

bunun için, sağda (im) kısımda 0 olmasını

$$6 - j(10^{-2}\omega - \frac{1}{\omega C})$$

$$6 - j(10^{-2}\omega - \frac{1}{\omega C})$$

$$-6j + \frac{10^{-2}}{C}$$


$$6 + j(10^{-2}\omega - \frac{1}{\omega C})$$

$$\frac{-36j - j \left(\frac{10^{-4}\omega}{C} - \frac{10^{-2}}{\omega C^2} \right)}{6 + j(10^{-2}\omega - \frac{1}{\omega C})} = 0 \Rightarrow \frac{36}{\omega C} + \frac{10^{-4}\omega}{C} - \frac{10^{-2}}{\omega C^2} = 0$$

$$\frac{36}{800\pi \cdot C} + \frac{10^{-4} \times (800\pi)}{C} - \frac{10^{-2}}{800\pi(C^2)} = \frac{0,0143}{C} + \frac{0,2513}{C} = \frac{3,9288 \times 10^{-6}}{C^2}$$

$$C = 15,832 \times 10^{-6} \Rightarrow C \approx 15,832 \text{ nF}$$

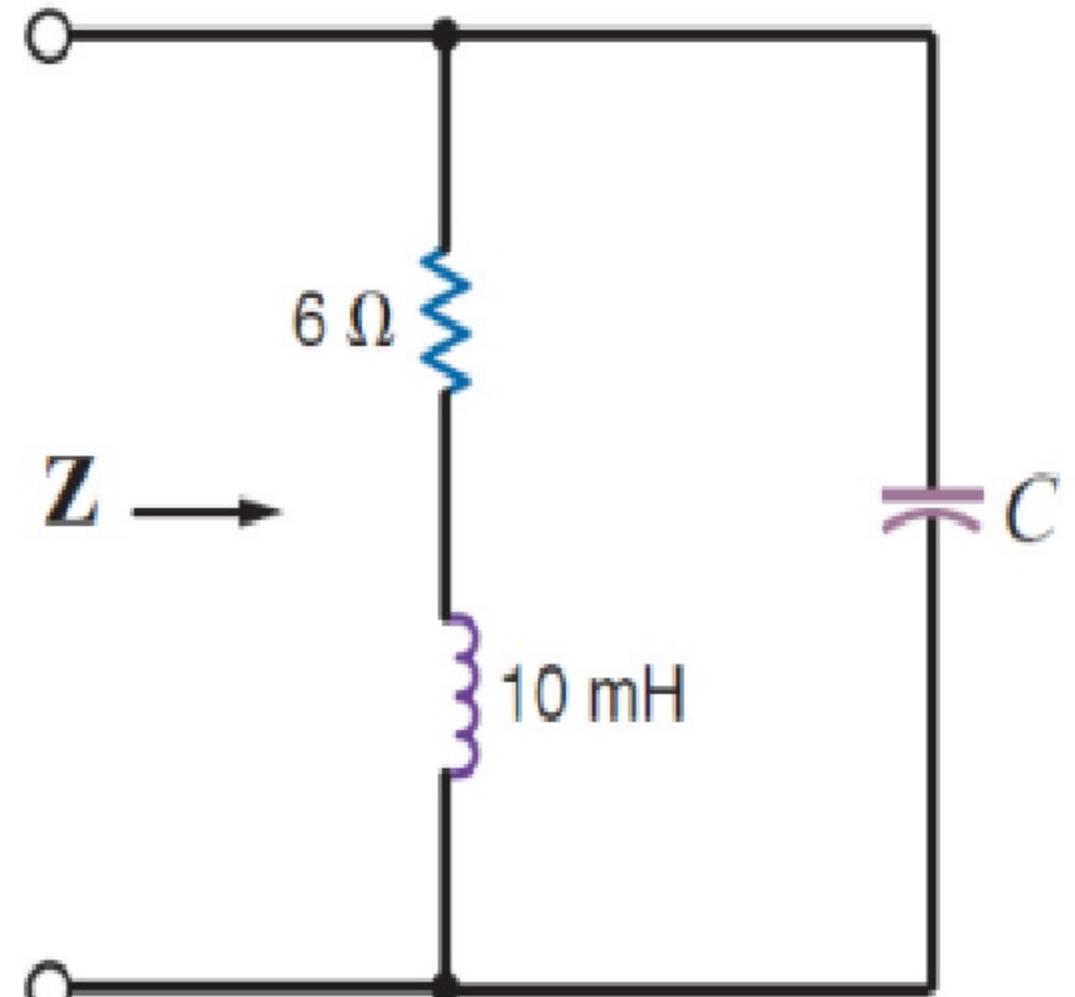- 8.18 The impedance of the network in Fig. P8.18 is found to be purely real at $f = 400 \text{ Hz}$. What is the value of C ?



8.31 Calculate $v_1(t)$ if $i_1(t) = 7 \cos 100t$ A and $i_2(t) = 3 \cos(100t + 45^\circ)$ in Fig. P8.31.

8.31



$$i_1(t) = 7 \cos 100t$$

$$i_2(t) = 3 \cos(100t + 45^\circ)$$

$$I_1 = 7 \angle 0^\circ$$

$$I_2 = 3 \angle 45^\circ$$

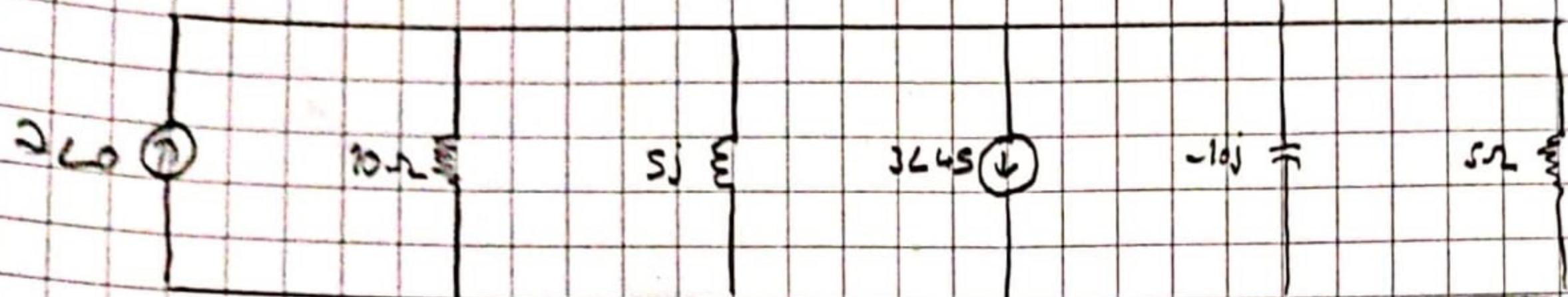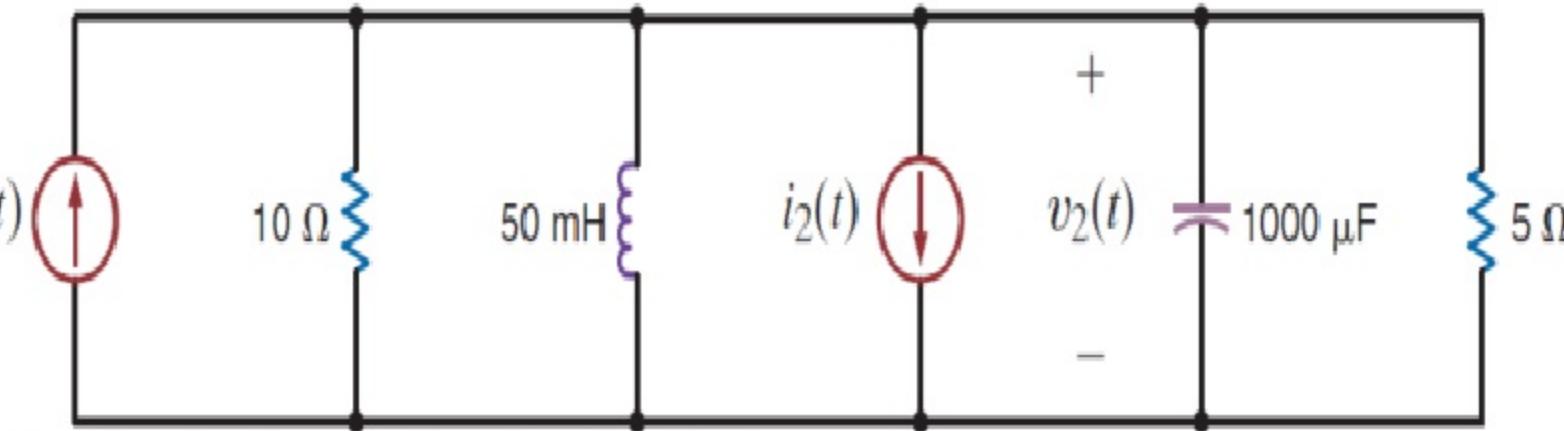
$$Z_L = (50 \cdot 10^{-3}) \cdot (100)j, Z_L = 5j, Z_C = \frac{-j}{\frac{10^3}{10^3} + \frac{10^{-6}}{10^2}}, Z_C = -10j$$



$$\frac{1}{10} + \frac{1}{5j} + \frac{1}{-10j} = \frac{1}{R_g}$$

$$\frac{3j+2}{10j} = \frac{1}{R_g}$$
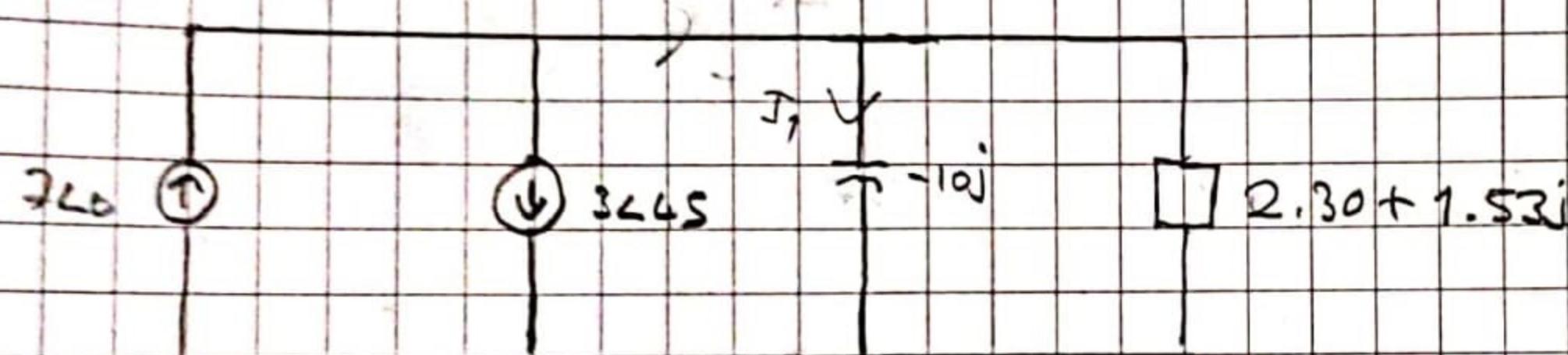
$$R_g = \frac{10j}{3j+2}, R_g = 2.30 + 1.53j$$



$$I_1 = (7 - 2.12 - 2.12j) \times \left(\frac{2.30 + 1.53j}{2.30 - 8.43j} \right)$$

$$I_1 = (4.88 - 2.12j) \times (-0.09 + 0.20j), I_1 = 0.12 + 1.60j$$

$$V_2 = I_1 \times (-10j), V_2 = -16 - 1.70j; V_2 = 16.09 \angle -6.05^\circ$$

$$V_2(t) = 16.09 (\cos 100t - 6.05)$$

8.31 Calculate $v_1(t)$ if $i_1(t) = 7 \cos 100t$ A and $i_2(t) = 3\cos(100t + 45^\circ)$ in Fig. P8.31.



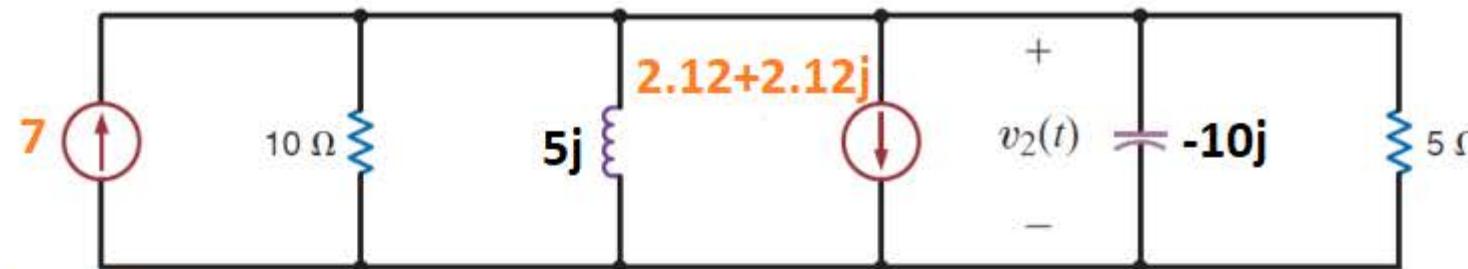


Figure P8.31

Source Transformation - Example

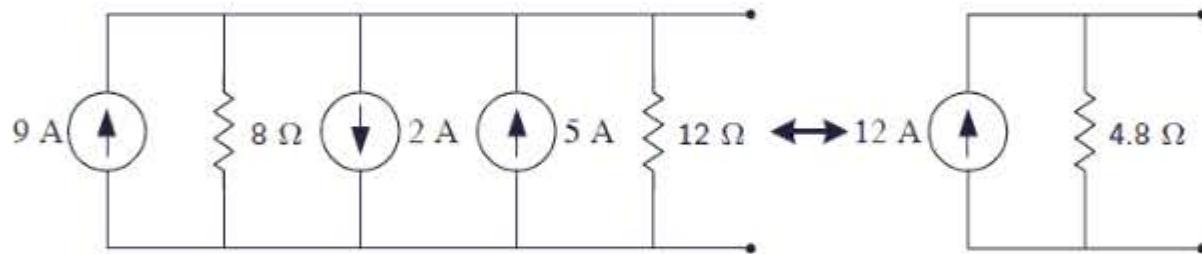


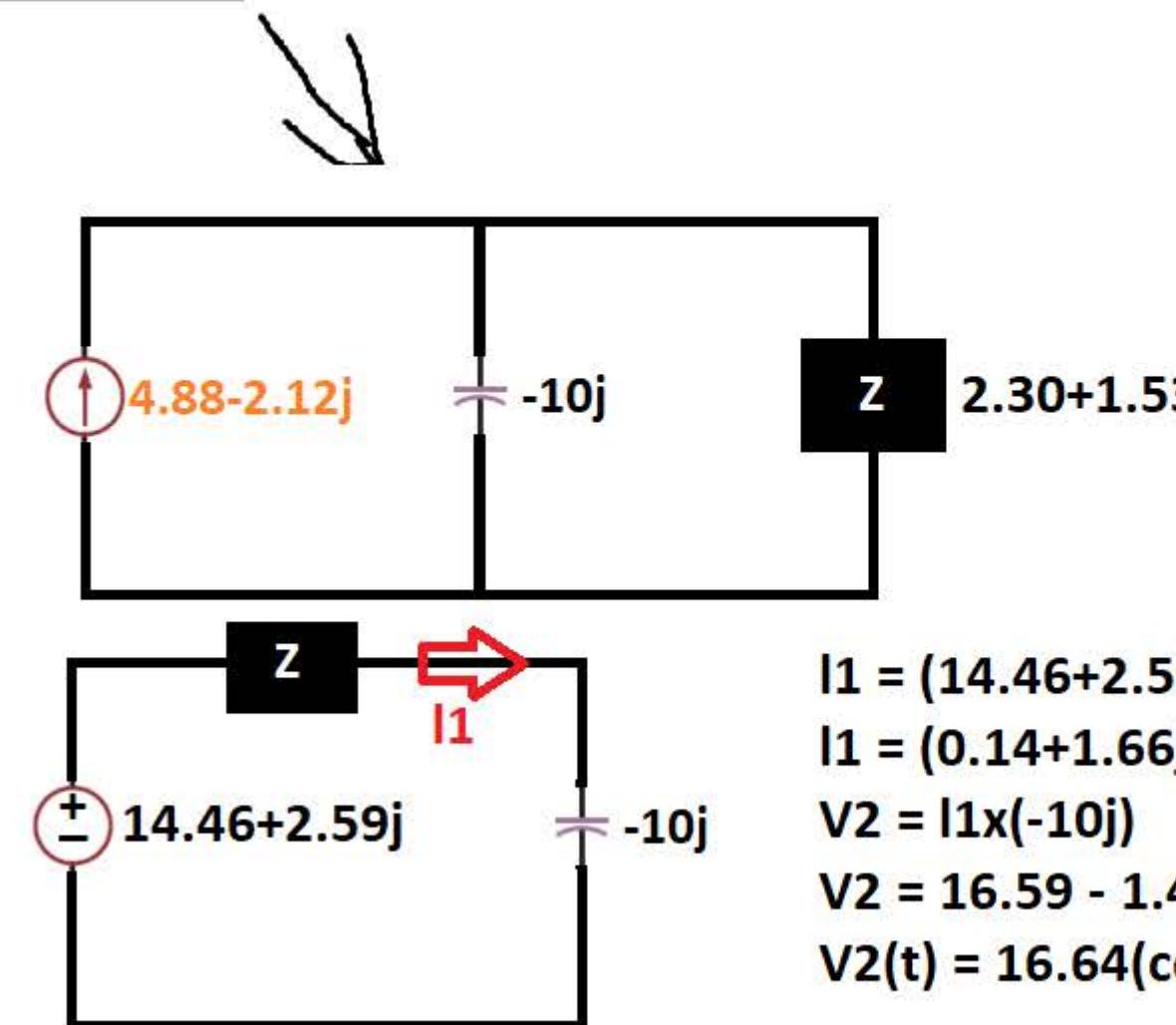- Recall: Current sources in parallel add
- Recall: The conductance of resistors in parallel adds
- Mixture of both in parallel also has an equivalent
 - Equivalent current source = sum of the currents
 - Equivalent resistance = parallel combination
- Proof possible by KCL (left as exercise)



$$\begin{aligned}
 I_1 &= (14.46+2.59j)/(Z-10j) \\
 I_1 &= (0.14+1.66j) \\
 V_2 &= I_1 \times (-10j) \\
 V_2 &= 16.59 - 1.40j \\
 V_2(t) &= 16.64(\cos 100t - 4.82)
 \end{aligned}$$

8.43

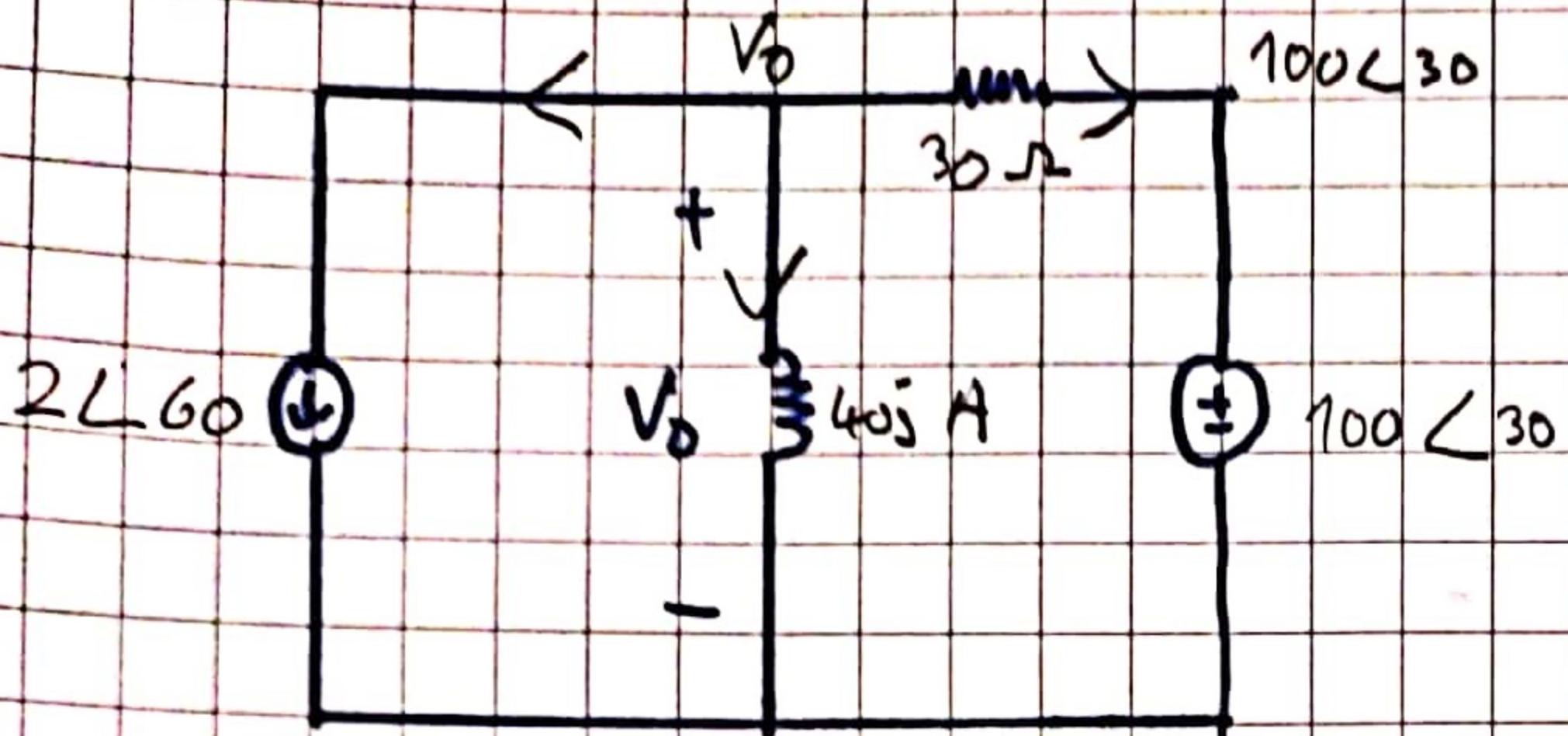

$$-2 \angle 60^\circ = \frac{3V_0 + 4V_0j - 4j(100 \angle 30^\circ)}{120j}$$

$$-120j(1+132j) = V_o(3+4j) - 4j(86.60 + 50j)$$

$$\frac{-120j + 203.6 + 346.4j - 200}{j+4j} = V_a$$

2261 88)
- 5253 ——————
 1

$$V_0 = 40.2 \angle 35^\circ$$

8.43 Find V_o in the network in Fig. P8.43.


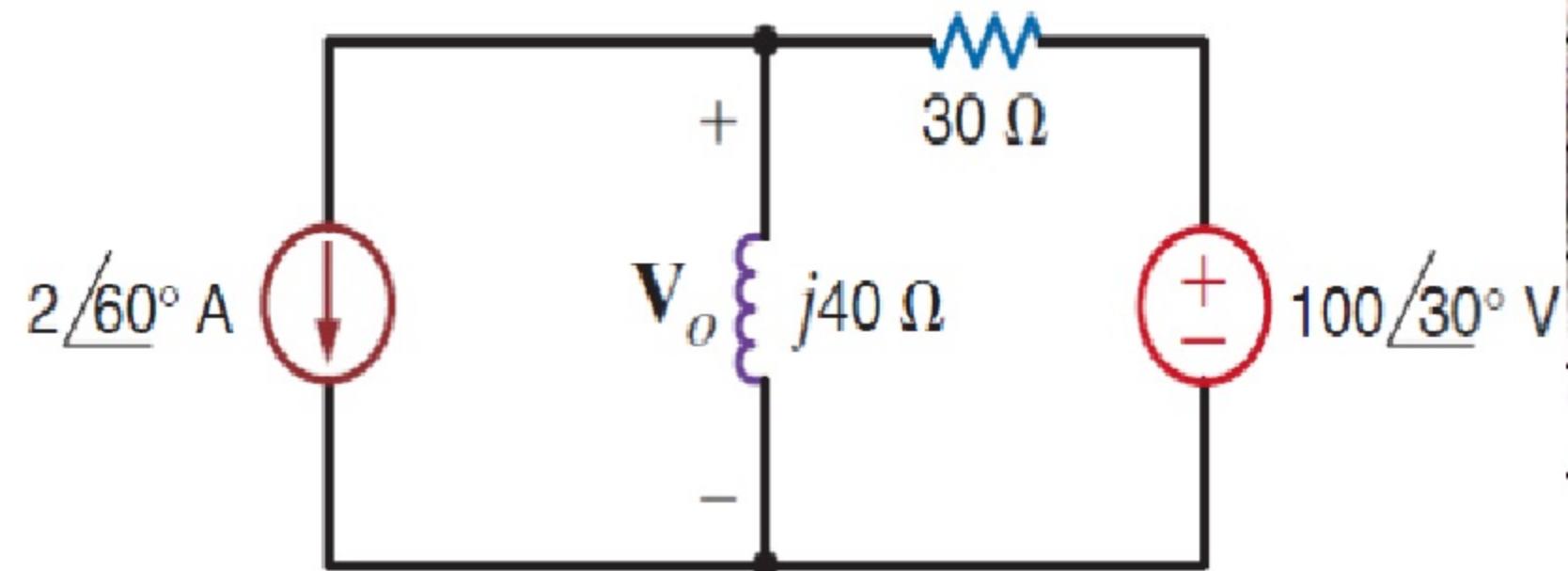


Figure P8.43

8.47

$$V_o = 4 \angle 45^\circ$$

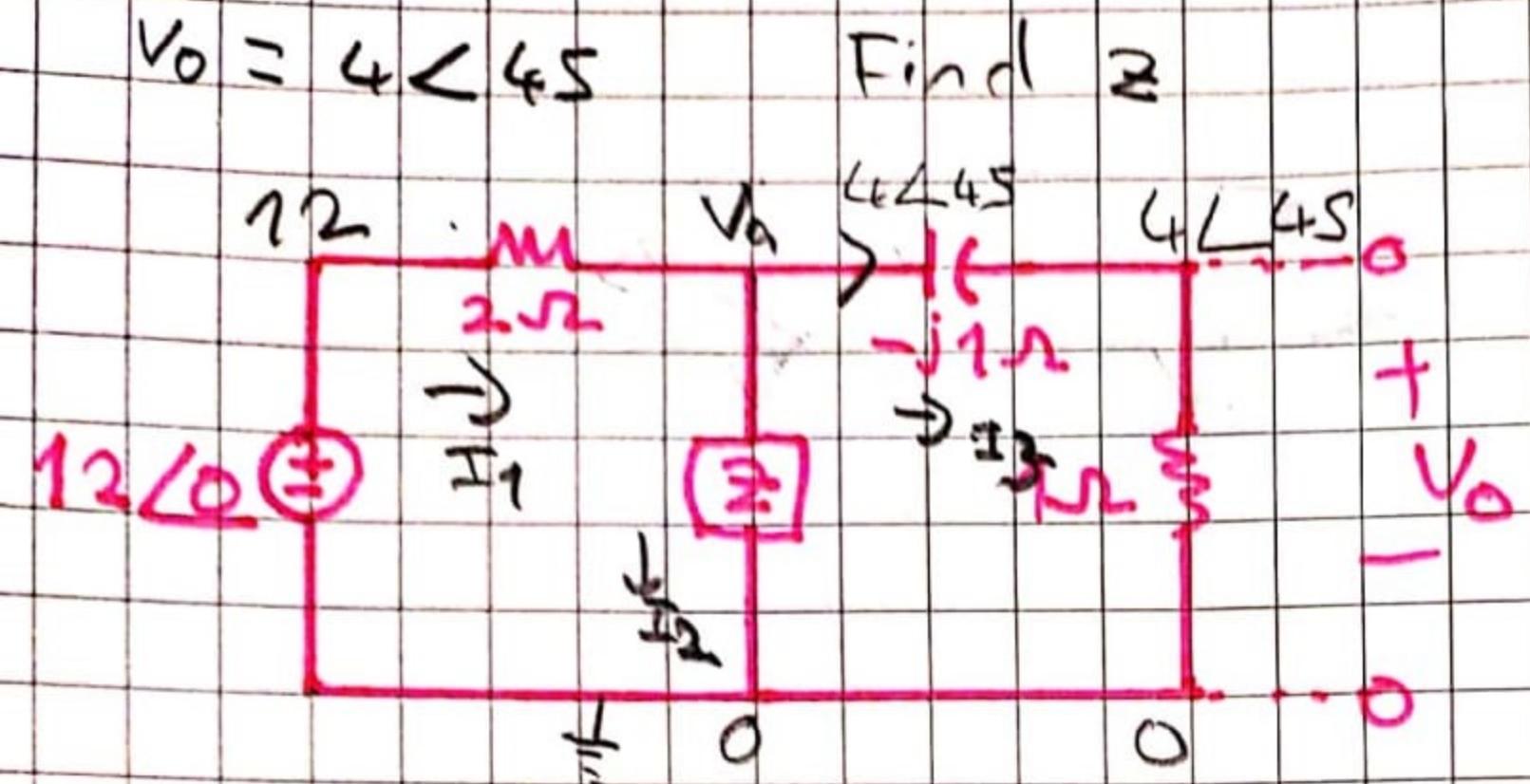


$$\frac{V_o - 0}{1 - j} = 4 \angle 45^\circ$$

$$V_o = (2.82 + 2.82j)(1 - j)$$

$$V_o = 5.64$$

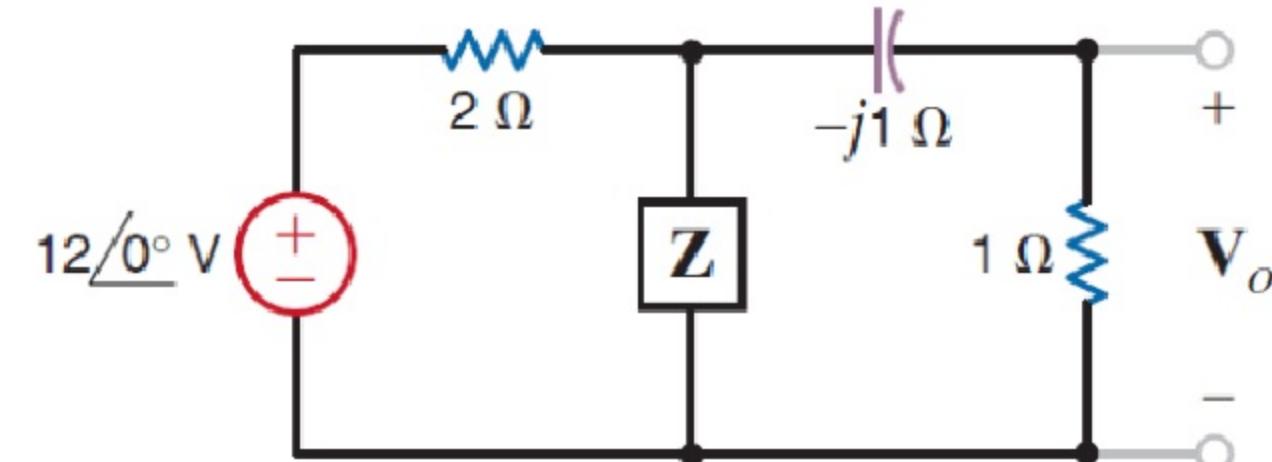8.47 In the network in Fig. P8.47, V_o is known to be $4/45^\circ$ V. Find Z .



$$(3.18 - 2.82 - 2.82j) = 0.36 - 2.82j = I_2$$

$$Z = \frac{5.64}{0.36 - 2.82j} = 0.25 + 1.96j$$

8.51

$$\text{4} = + \quad \text{6} = -$$

$$\frac{(V_1 - 12\angle 0)}{1-j2} + 2\angle 0 A + \frac{V_1}{j2} + \frac{V_1 - V_2}{1+j2} = 0$$

(1)

$$V_1 - 12 + 2 + V_1 + V_1 - V_2 = 0 \Rightarrow V_2 = 3V_1 - 10$$

$$-\frac{(V_1 - V_2)}{1+j2} - \frac{V_2}{j} - 4\angle 0 = 0 \Rightarrow -\frac{(V_1 - V_2)j + V_2}{j} = 4$$

(2)

$$4j = -2V_1 j - 10j + 10 - 3V_1 \Rightarrow 14j - 10 = V_1(2j - 3)$$


$$V_1 = \frac{14j - 10}{2j - 3} \Rightarrow V_1 = \frac{\sqrt{(14)^2 + (10)^2}}{\sqrt{(2)^2 + (3)^2}} \angle \tan^{-1} \frac{14}{10} - \tan^{-1} \frac{3}{2}$$

$$V_1 \approx 4.231 \angle 20.33^\circ$$


(3)

$$I_o = 4.231 \angle 20.33^\circ$$

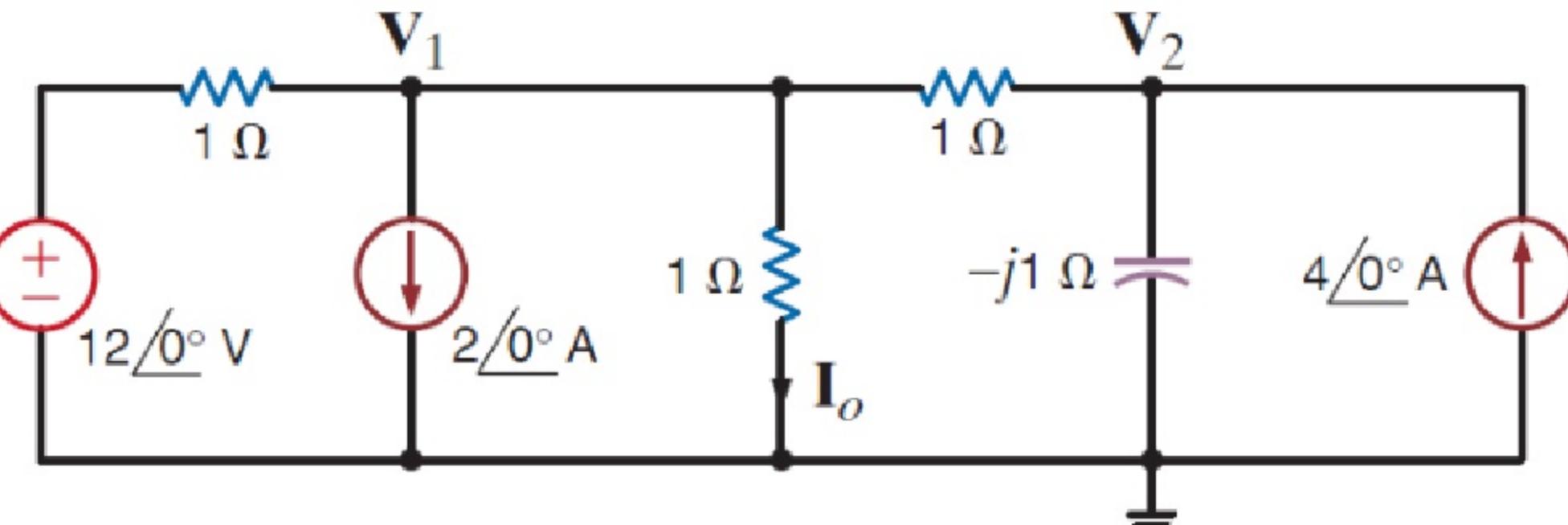
8.51 Using nodal analysis, find I_o in the circuit in Fig. P8.51.



8.68

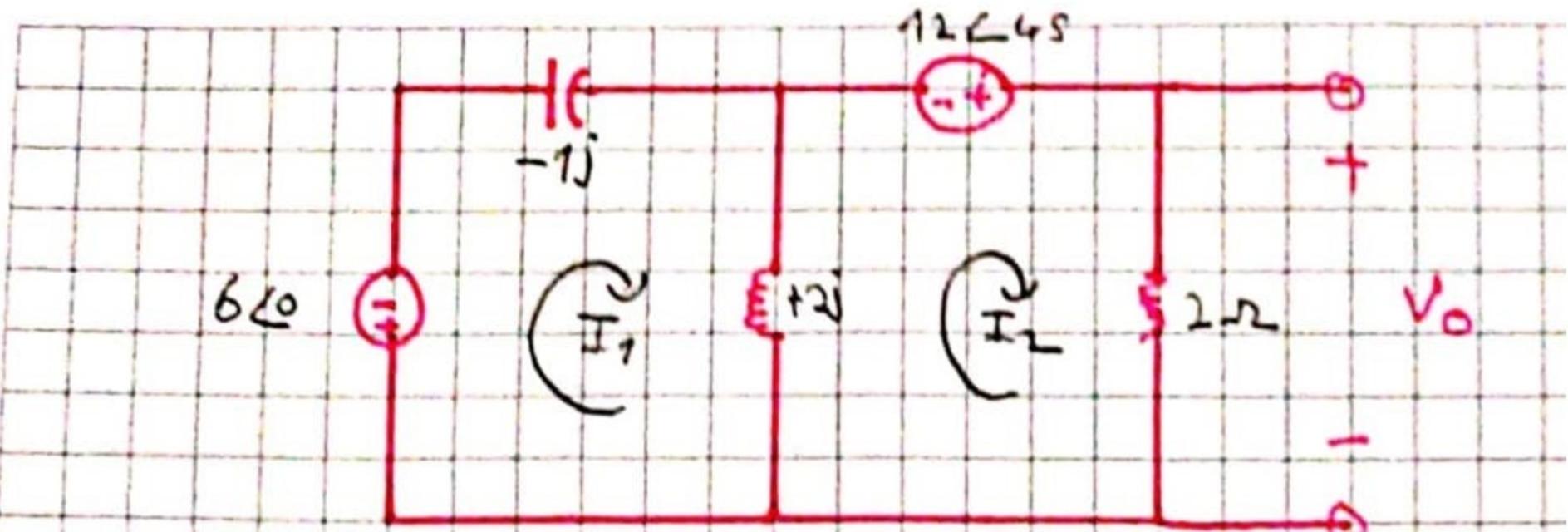

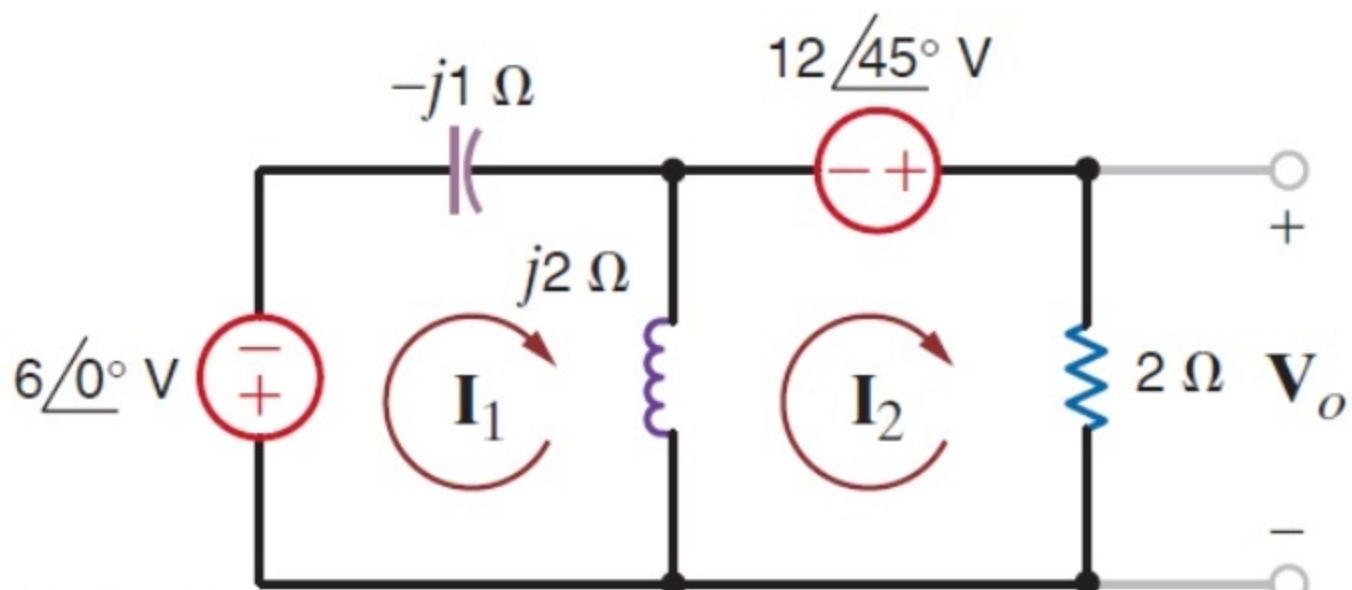8.68 Use mesh analysis to find V_o in the circuit shown in Fig. P8.68.



$$6 \angle 0^\circ - jI_1 + 2jI_1 - 2jI_2 = 0$$

$$j(-I_1 + 2I_2) = 6$$

$$2I_2 = V_o$$

$$2I_2 j - 6 = I_1 j$$

$$2jI_2 - 2jI_1 - 12 \angle 45^\circ + 2I_2 = 0$$

$$12 \angle 45^\circ = 8.48 + 8.48j$$

$$j(2I_2 - 2I_1 - 8.48) - 8.48 + 2I_2 = 0$$

$$8.48 = 2I_2 j - 2I_1 j - 8.48j + 2I_2$$

$$8.48 = 2I_2 j - 4I_2 j + 12 - 8.48j + 2I_2 , 2I_2 j \sim 2I_2 = 3.52 - 8.48j$$


$$I_2 = \frac{3.52 - 8.48j}{2j - 2} = \underline{\underline{0.18 \angle -67.45}}$$

$$I_2 = 3.25 \angle -22.45$$

$$V_o = 2 \angle 0^\circ \times (I_2)$$

$$\boxed{V_o = 6.5 \angle -22.45}$$

8.72

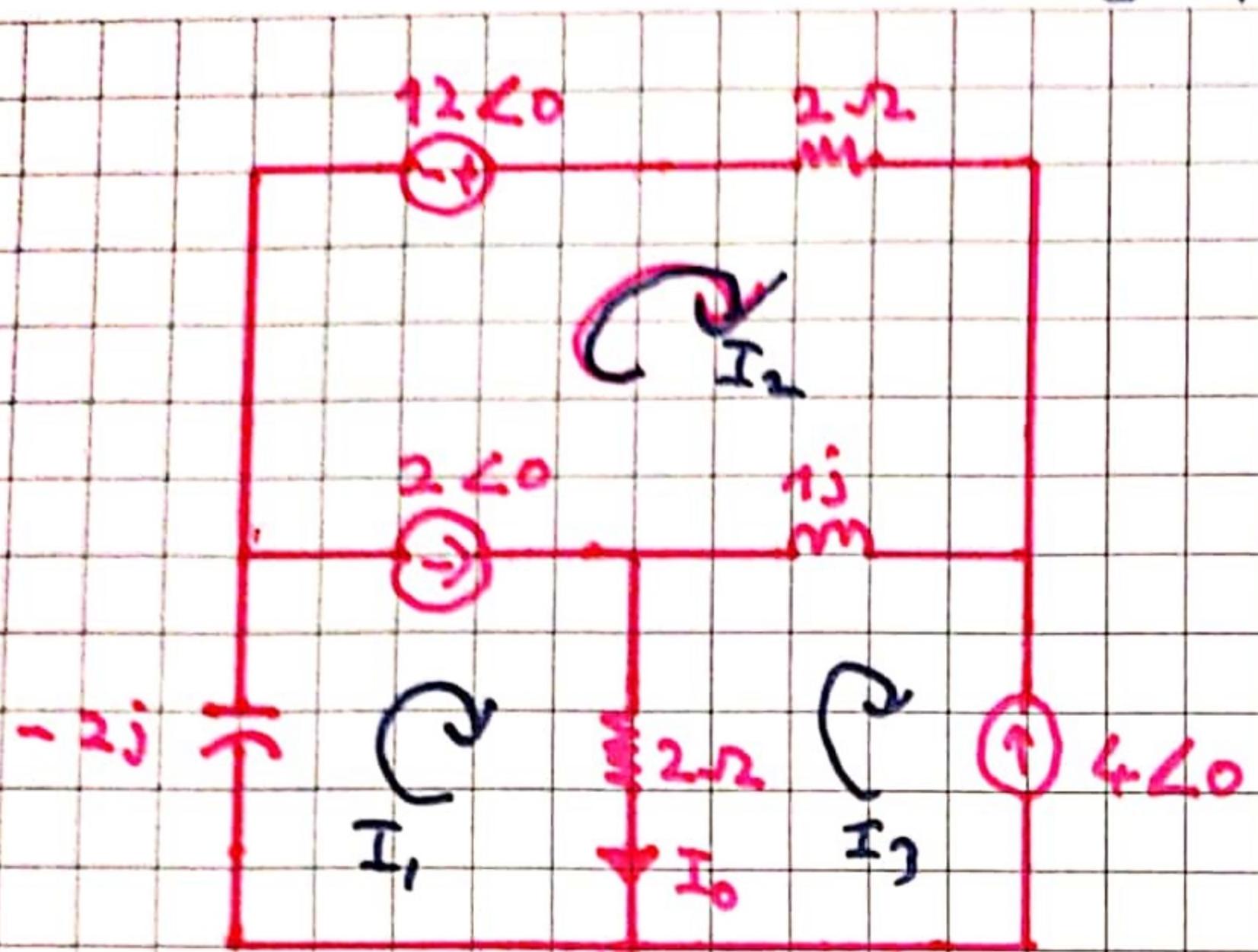

$$I_1 - I_2 = I_o$$

$$I_3 = -4$$

$$I_1 - I_2 = 2$$

$$I_2 = I_1 - 2$$

I_1 ve I_2 supermesh

$$-2I_{1j} - 12 + 2I_{2j} + 2I_{2j} + 4j + 2I_1 + 8 = 0$$

I_2 yi I_1 cihfindeler yozulmam


$$-2I_{1j} - 12 + 2I_1 - 4 + 2I_{1j} - 4j + 4j + 2I_1 + 8 = 0$$

$$4I_1 - 8 = 0$$

$$I_1 = 2$$


$$I_o = 6A = 6\angle 0^\circ A$$

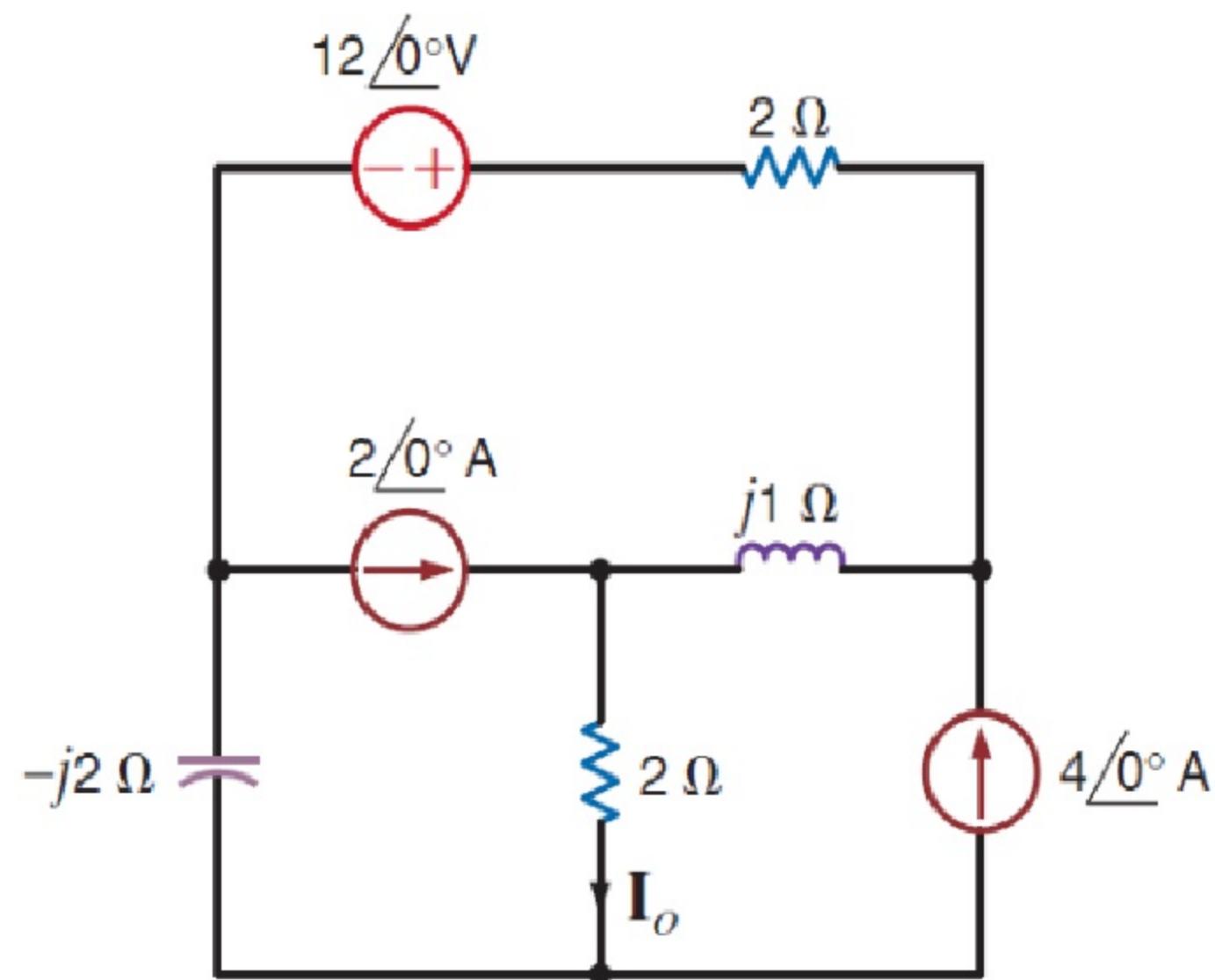8.72 Using loop analysis, find I_o in the network in Fig. P8.72.



8.80

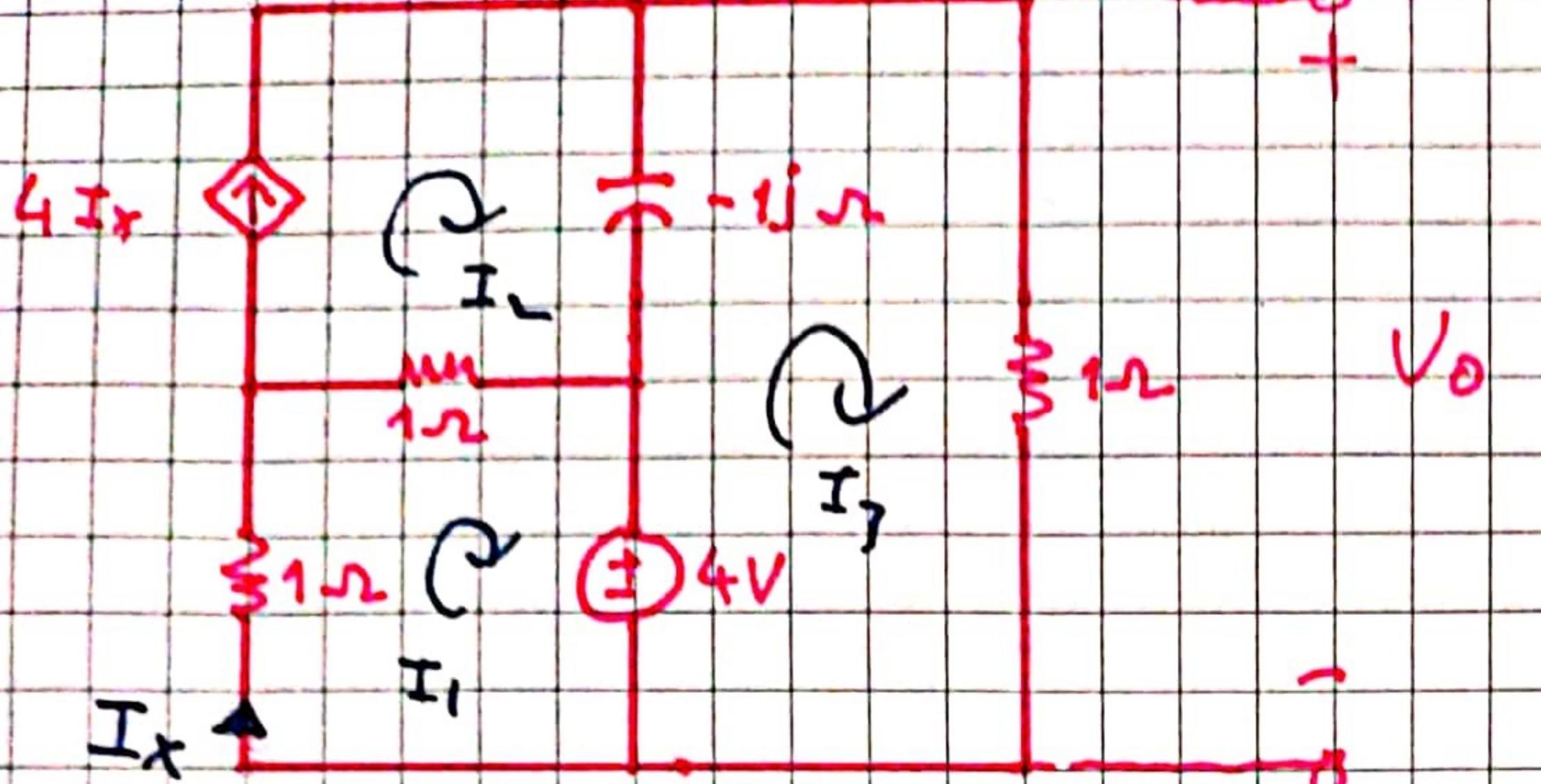8.80 Use loop analysis to find V_o in the circuit in Fig. P8.80.



ΣV

$$-4V = I_1 + I_1 - I_2$$

$$\boxed{I_x = I_1 \quad I_2 = 4I_x}$$

$$-4 = 2I_1 - I_2$$

$$-4 = 2I_x - 4I_x$$

$$\begin{aligned} I_2 &= 8 \\ I_1 &= 2 \end{aligned}$$

$$I_x = 2$$

$$I_3 = \frac{4-8j}{1-j} \quad (1+j)$$

$$\boxed{V_o = 6-2j}$$

$$\Rightarrow \frac{4-8j+4j+8}{2}$$

$$\Rightarrow \frac{12-4j}{2} \Rightarrow 6-2j$$

$$\boxed{V_o = 6.32 \angle -18.43^\circ}$$


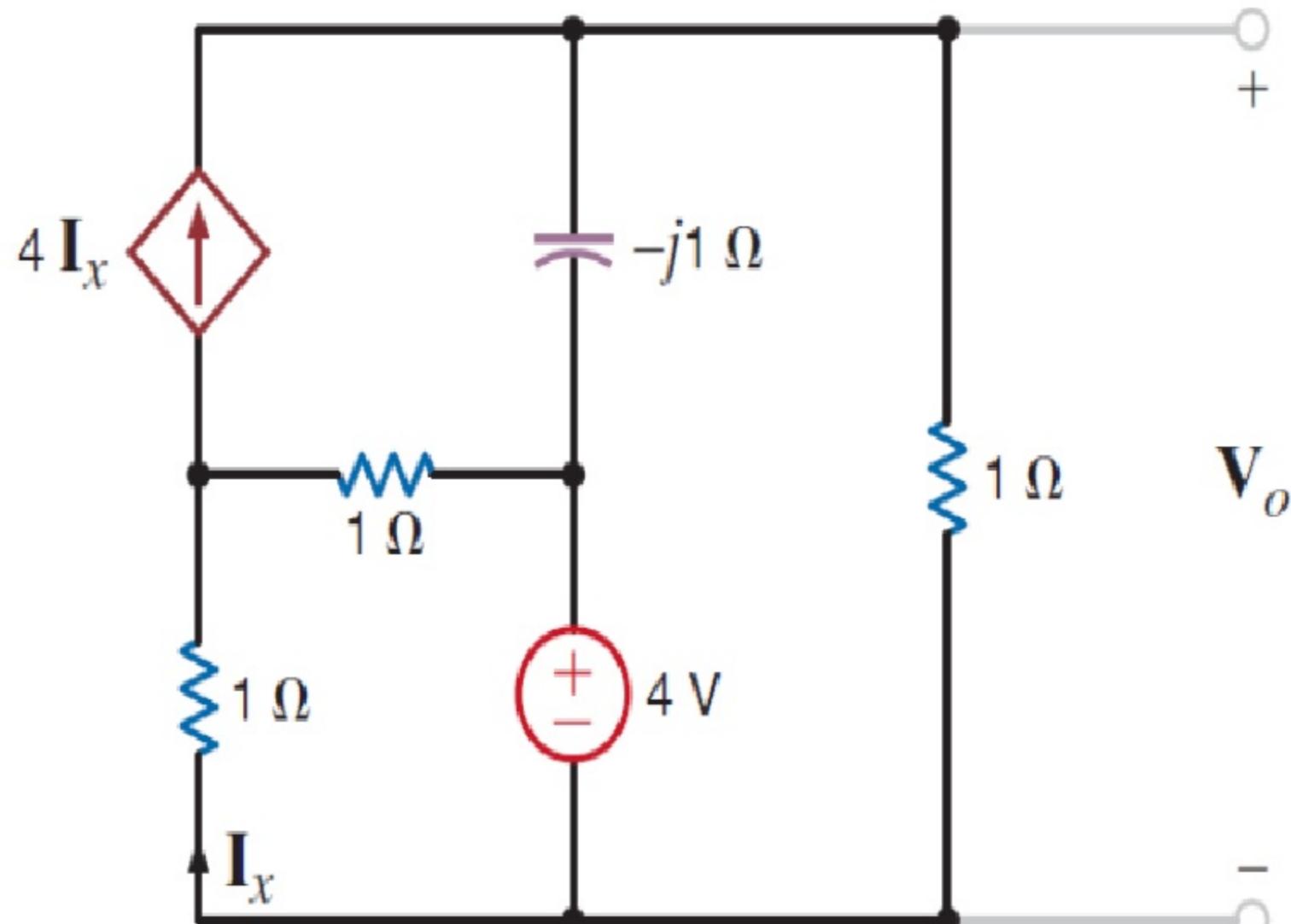
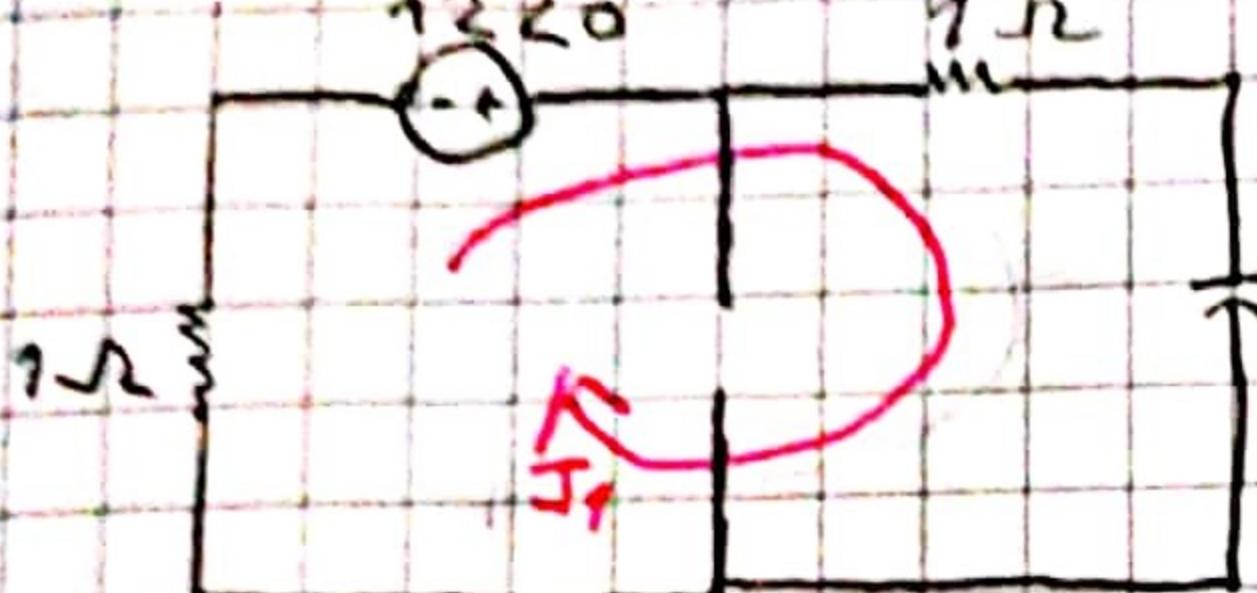


Figure P8.80

8.85

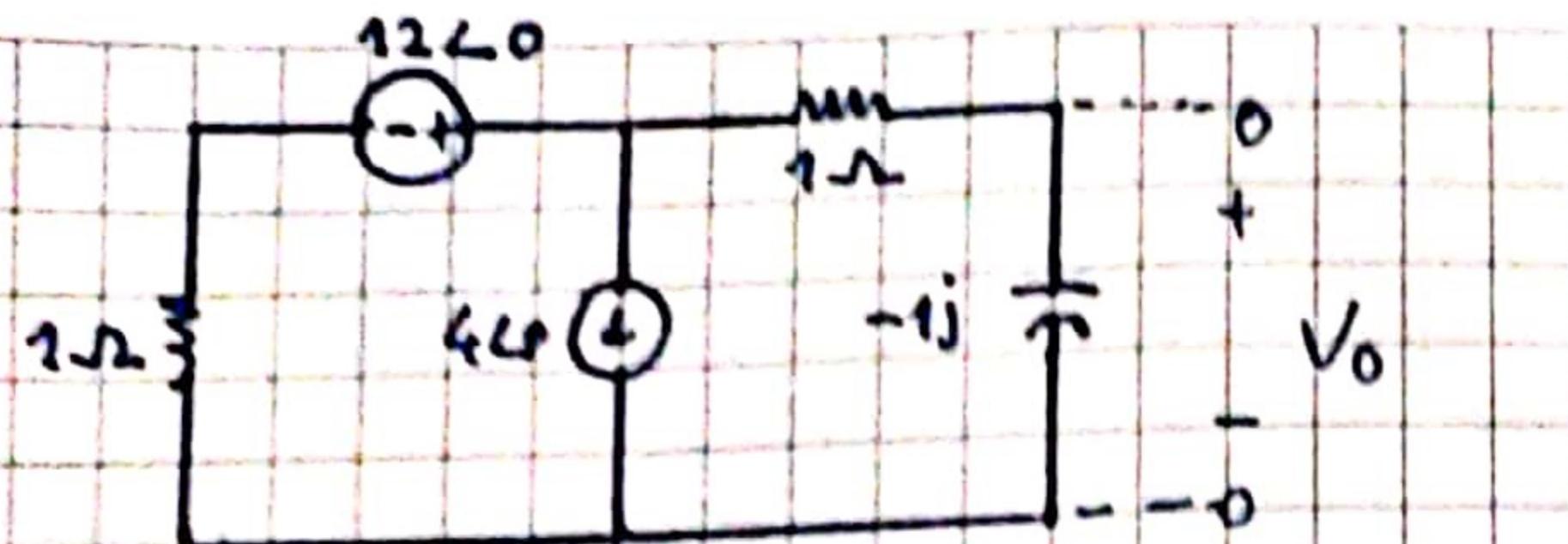

ilk basta alamıca gibi close


Mesh alamıca

$$1I_1 - 12 + 1I_2 - 1I_{1,j} = 0$$

$$12 = I_1(2-j) \Rightarrow I_1 = \frac{12}{2-j} \\ (2+j)$$

$$I_1 = \frac{24+12j}{5} \Rightarrow 4.8 + 2.4j$$
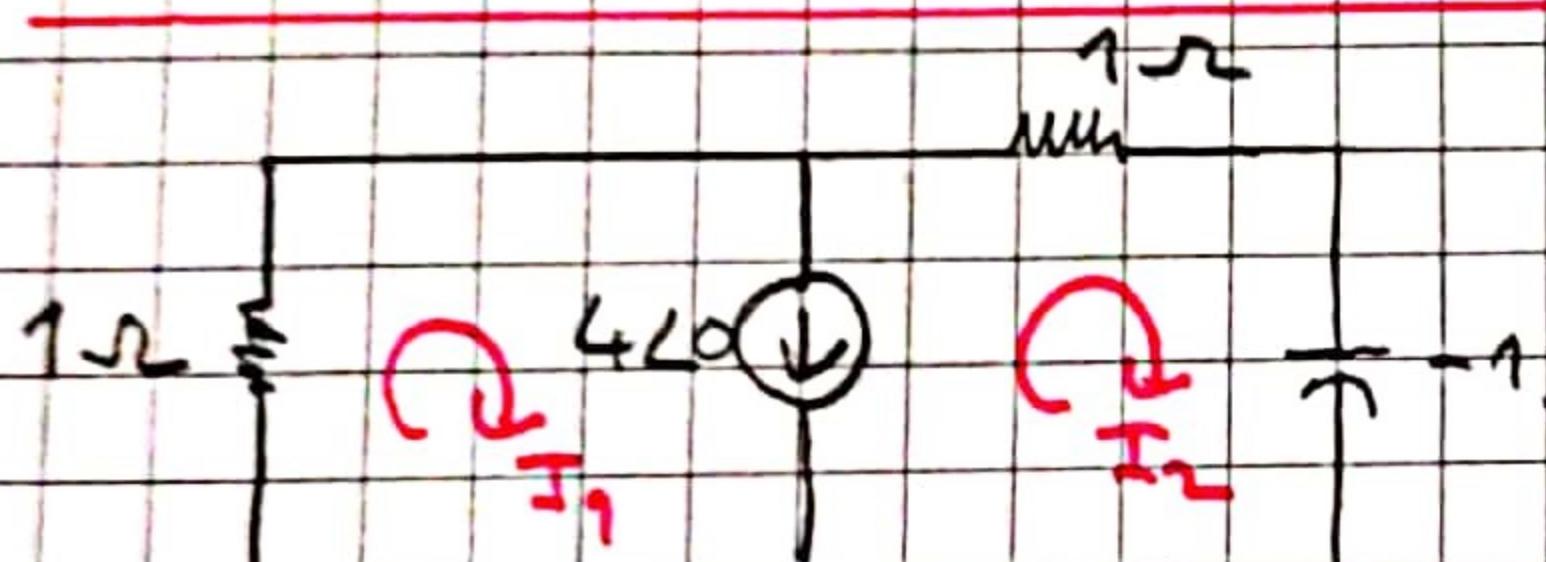
$$V_o' = -1j \times I_1 = -4.8j + 2.4 \Rightarrow V_o' = 2.4 - 4.8j$$



Görülmüş yolu da close

Supermesh alamıca

$$I_1 + I_2 - I_{2,j} = 0, \quad I_1 - I_2 = 4$$

||


$$4 + 2I_2 - I_{2,j} = 0 \Rightarrow I_2(2-j) = -4 \Rightarrow I_2 = \frac{-4}{2-j} \\ (2+j)$$

$$I_2 = \frac{-8-4j}{5} \Rightarrow I_2 = -1.6 - 0.8j \Rightarrow V_o' = -1j \times (-1.6 - 0.8j)$$

$$V_o' = 1.6j - 0.8, \quad [V_o'' + V_o' = V_o], \quad V_o = -3.2j + 1.6$$

$$V_o = 1.6 - 3.2j$$

$$V_o = 3.57 \angle -63.43^\circ$$

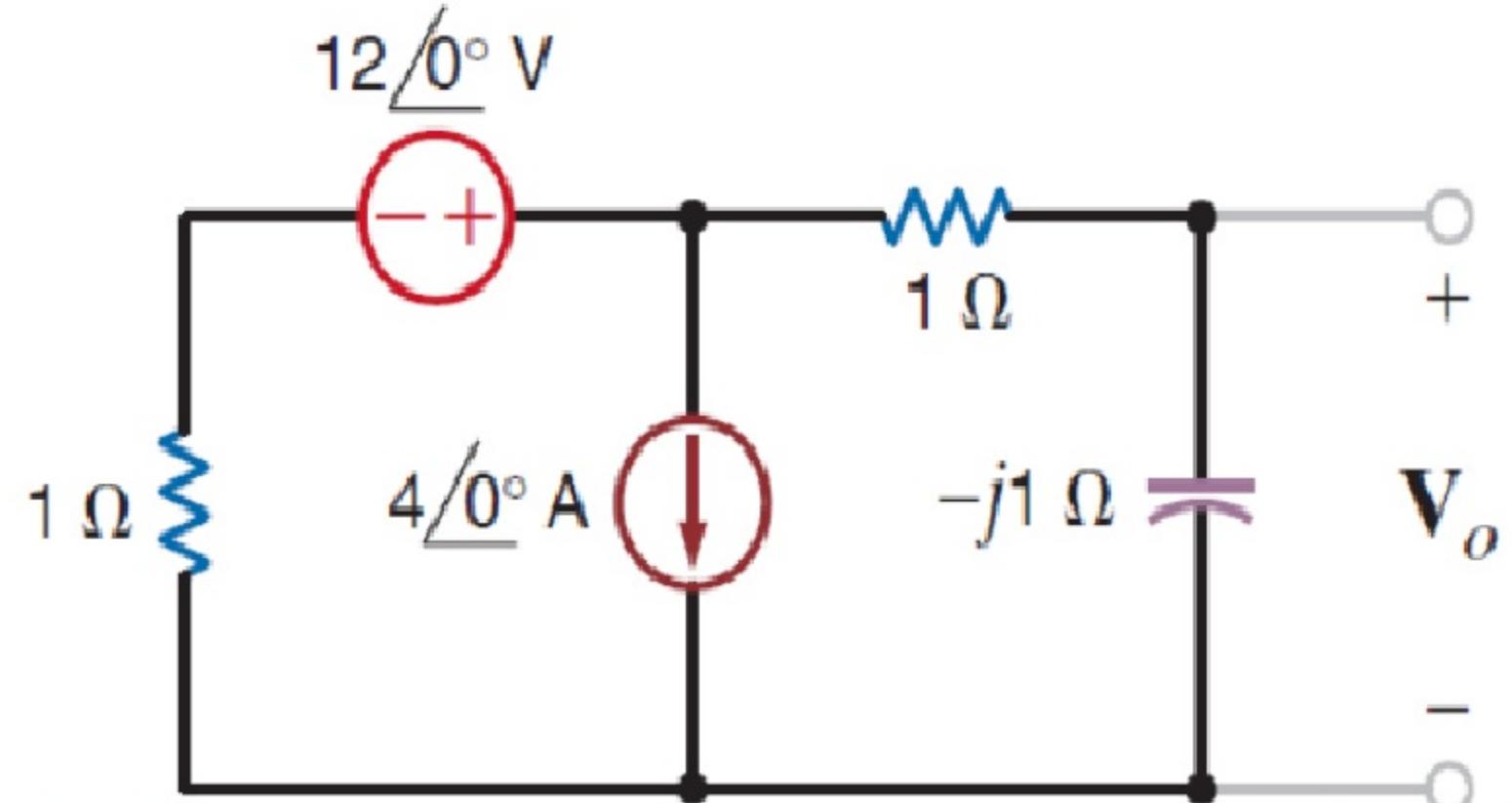

8.93 Use source exchange to find the current I_o in the network in Fig. P8.93.


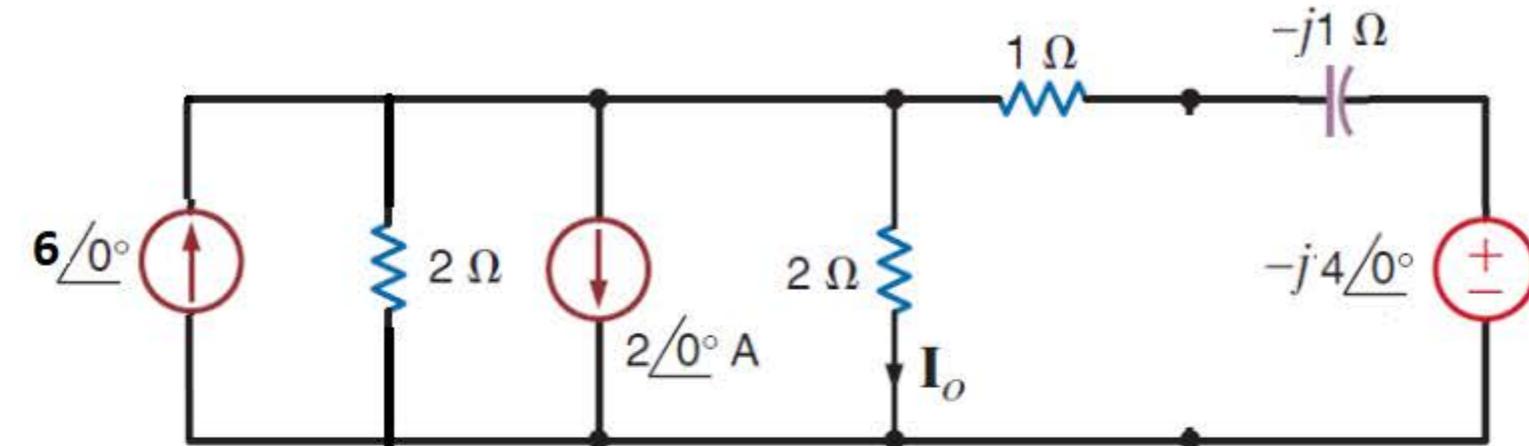
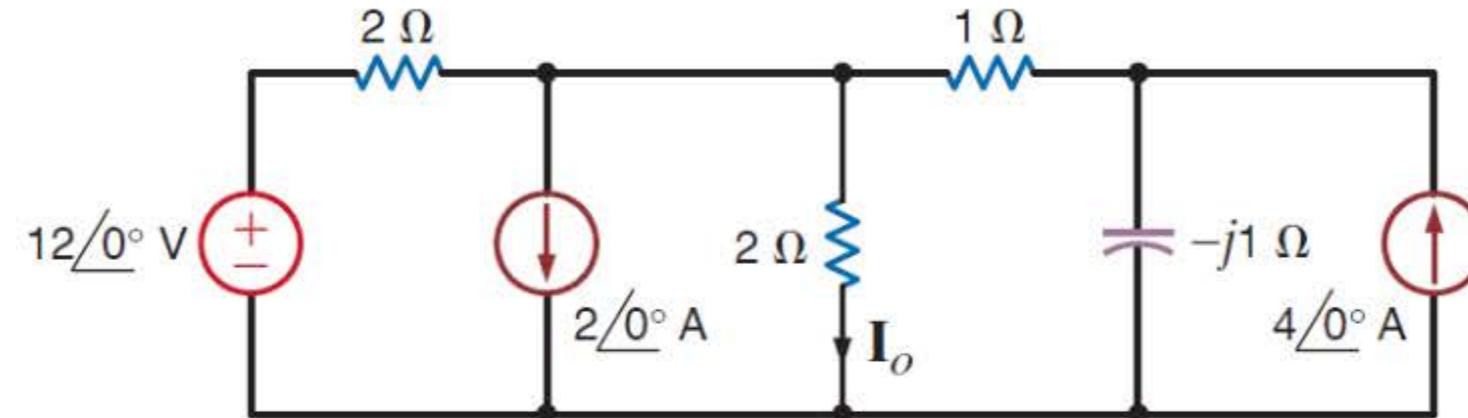
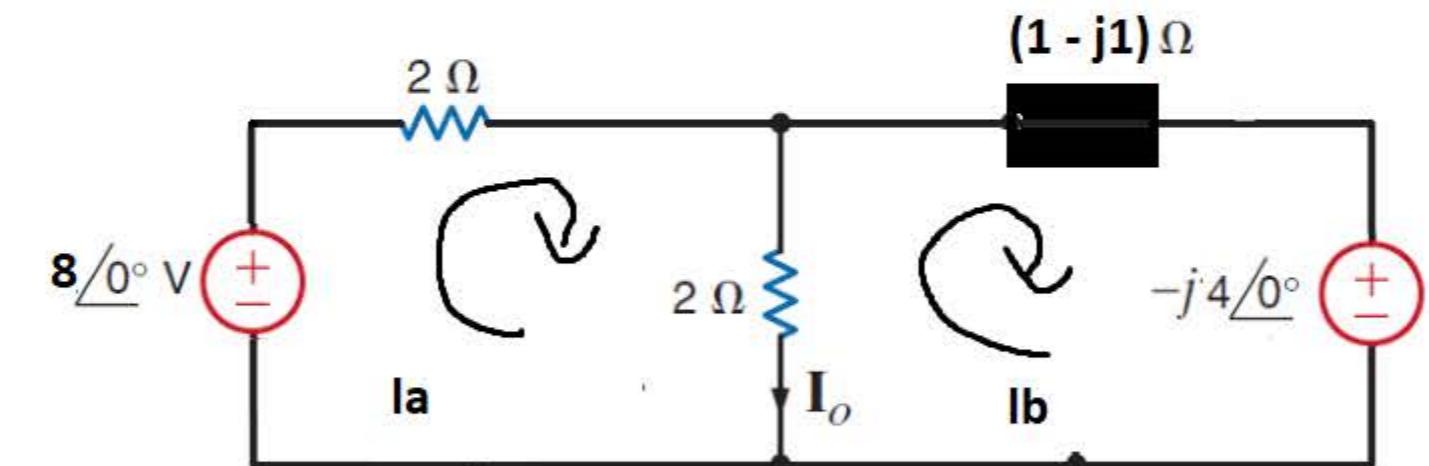


Figure P8.93

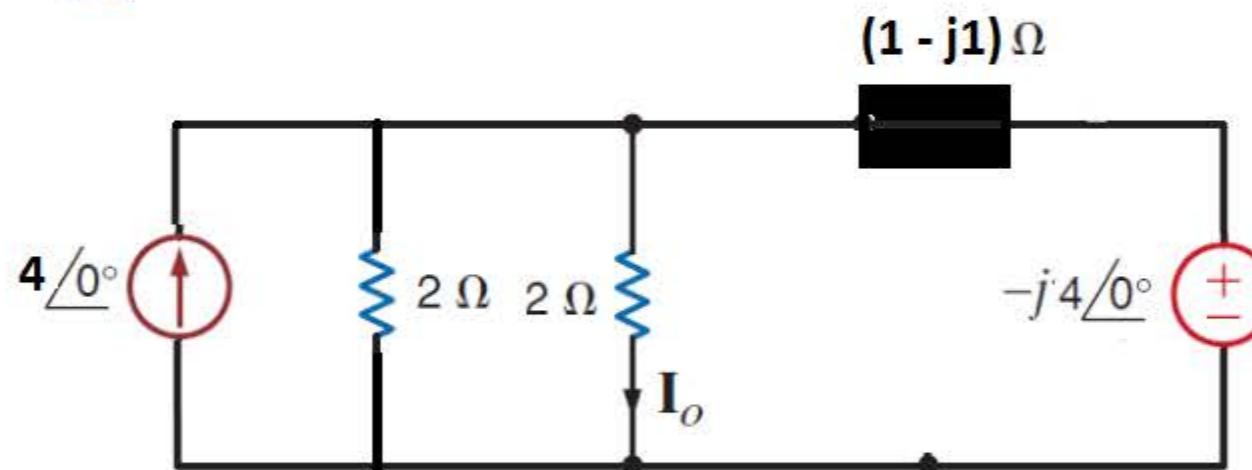

$$I_o = I_a - I_b$$



$$I_a \text{ için mesh: } 8 = 2I_a + 2I_a - 2I_b , \quad 4 = 2I_a - I_b$$

$$I_b \text{ için mesh: } 4j = I_b - I_b j + 2I_b - 2I_a$$

$$(I_b \text{ denkleminde } I_b \text{ yerine } 2I_a - 4 \text{ yazalım}) \quad 4j = 2I_a - 4 - 2I_a j + 4I_a - 8 - 2I_a , \quad 12 = I_a (4 - 2j) \quad 12/(4 - 2j) = I_a \quad 2 \text{ tarafını da } (4 + 2j) \text{ ile çarpıyorum}$$


$$I_a = 2.4 + 1.2j \text{ geldi} \quad 4 = 2I_a - I_b \text{ de yerine yerleştirelim} \quad 0.8 + 2.4j = I_b \text{ geldi} , \quad I_o(t) = 1.6 - 1.2j \quad I_o = 2\angle -36.86$$

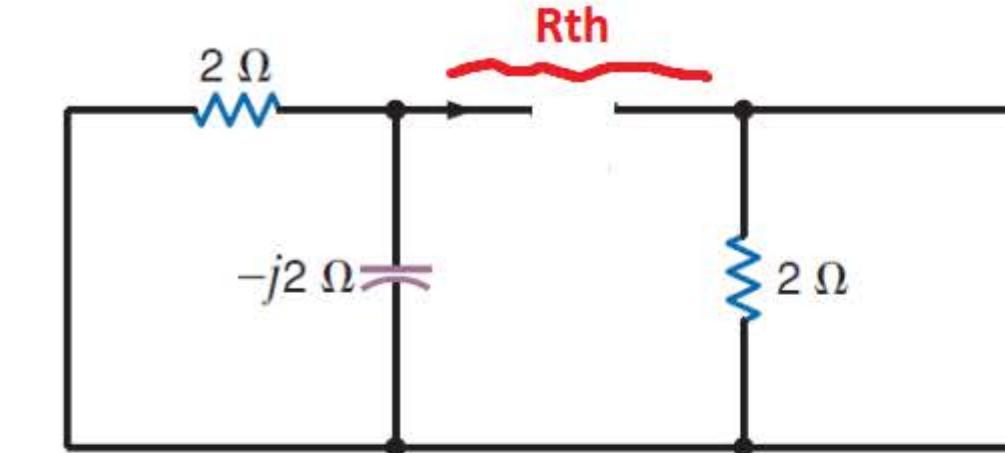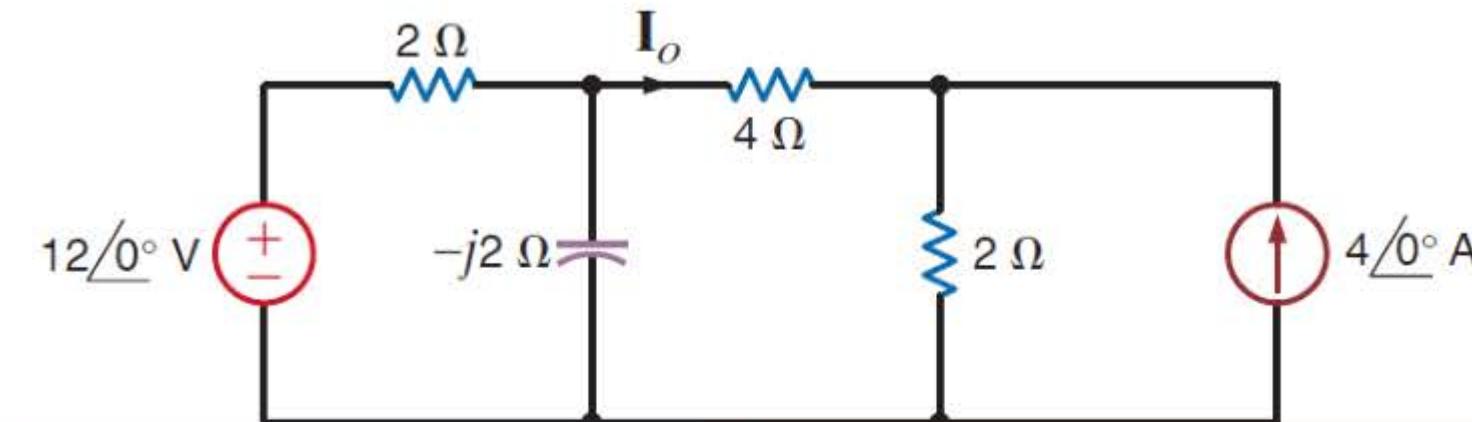8.103 Use Thévenin's theorem to find I_o in the network in Fig. P8.103.



$$R_{th} = (2 // -j2) + 2$$

$$R_{th} = 3 - j$$

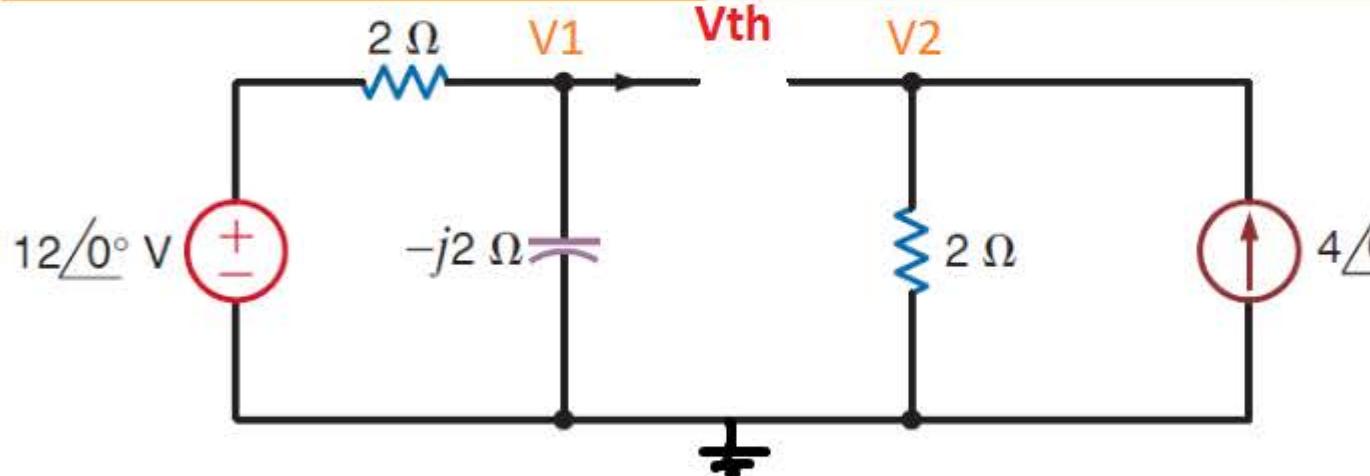


$$V_2 = 4A \times 2\text{ohm} = 8V$$

V_1 'i bulabilmek için $-j2$ üzerinden geçen akımı bulmamız lazım bu yüzden mesh alalım
 $-12 + 2I_a - j2I_a$
 $I_a(2-2j)=12$, $I_a = 6/(1-j)$, $I_a = 3 + 3j$, $I_a \times (-j2) = V_1$ $-6j + 6 = V_1$ geldi

$V_1 - V_2$ de bana V_{th} i verir

$$-6j + 6 - 8 = -2 - 6j \quad V_{th} = -(2+6j) \text{ geldi}$$



$$R_{th} = 3 - j$$

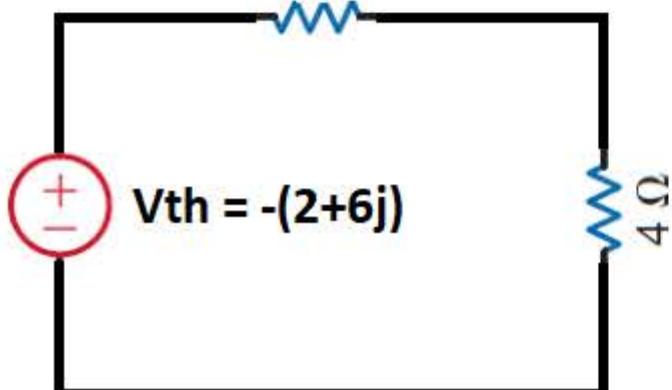

devrenin akımı I_o a eşit olacaktır.
 $(-2-6j) / 7-j = -0.16 - 0.88j$


$$I_o = -0.16 - 0.88j$$

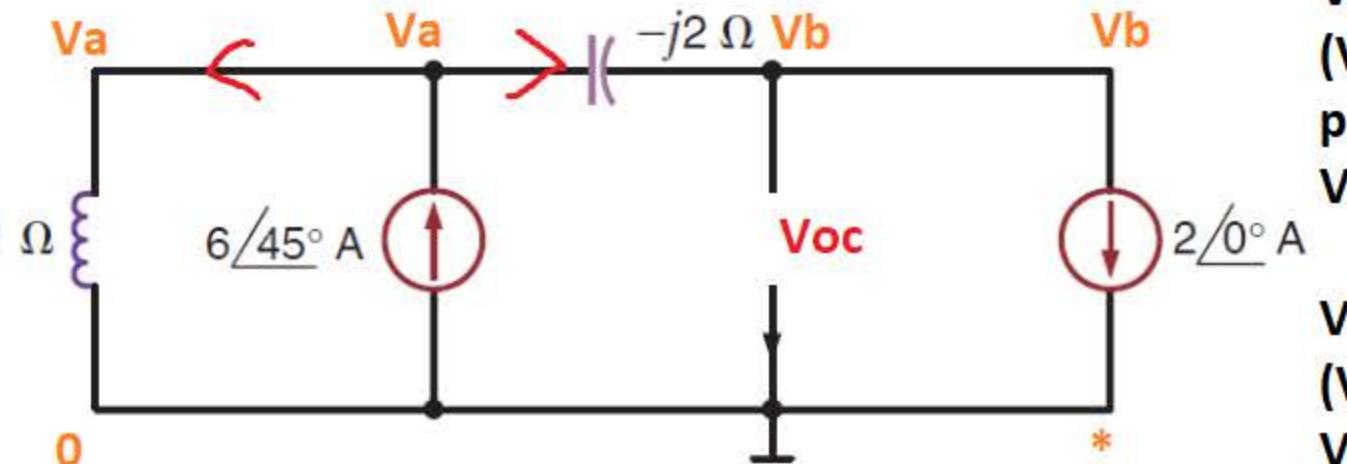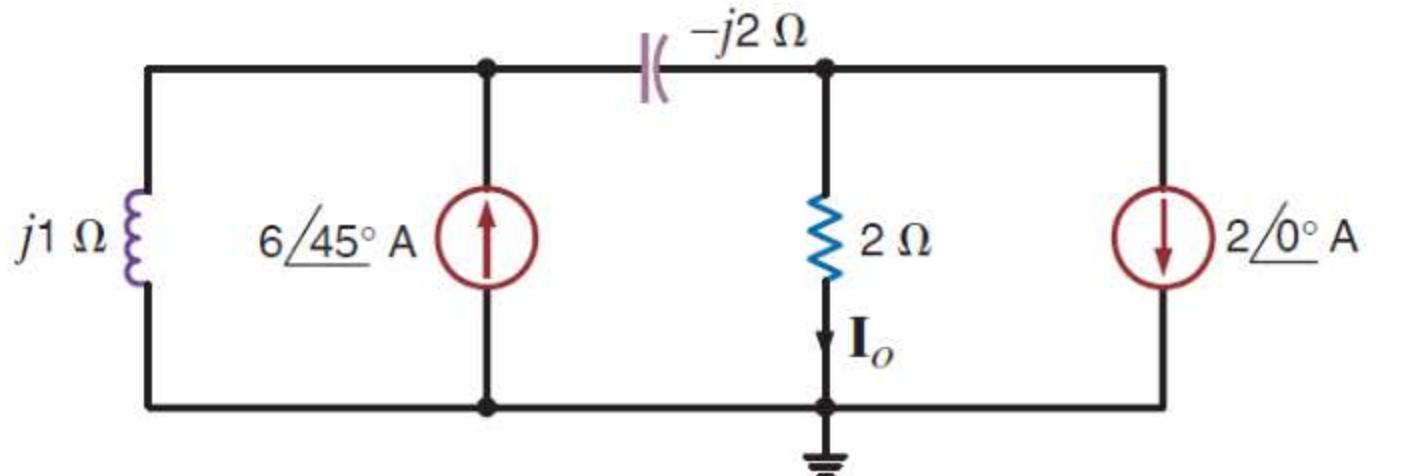8.114 Find I_o in the network in Fig. P8.114 using Norton's theorem.



V_a için mesh alalım , $G = -$, $\dot{C} = +$
 $(V_a/1j) - (4.24+4.24j) + ((V_a-V_b)/-2j) = 0$
paydaları $-2j$ de birleştirince
 $V_a+V_b = 8.48j - 8.48$ geldi

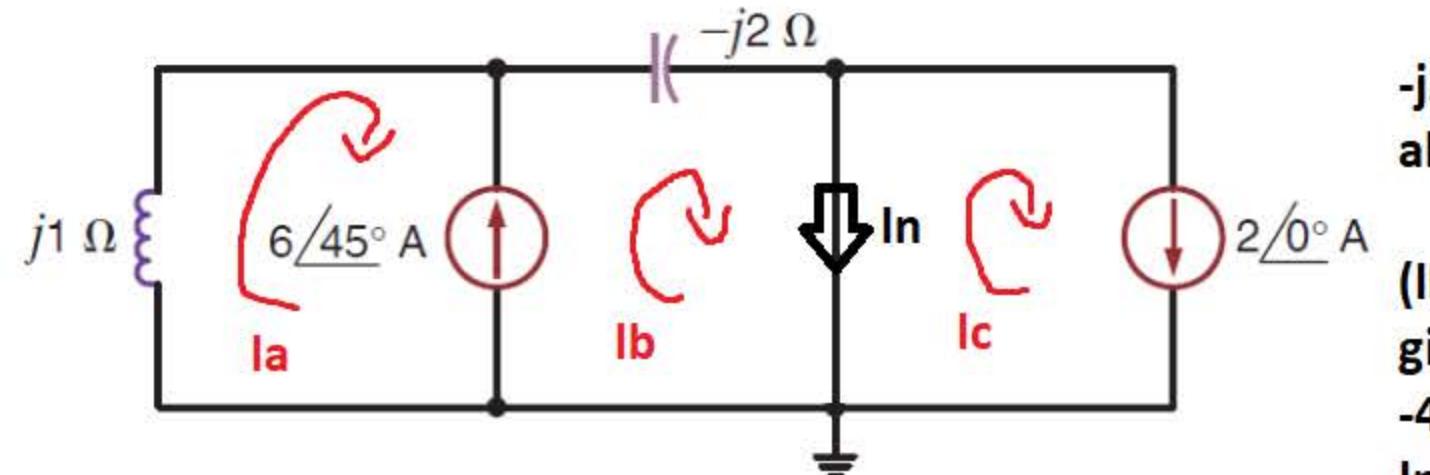V_b için mesh
 $(V_a-V_b/2j) + 2 = 0$, $V_a - V_b = -4j$
 $V_b = 6.24j - 4.42$
 $V_{oc} = V_b = 6.24j - 4.42$



$$I_b - I_a = 4.24 + 4.24j, \quad I_b - I_c = I_n, \quad I_c = 2$$

$-j2$ üzerinden geçen akımı bulmak için
akım bölgüsü uygulayalım


$$(I_b - I_a) \times (1j / -1j) = -4.24 - 4.24j \text{ geldi}$$

giren akım çıkan akımlara eşittir

$$-4.24 - 4.24j = 2 + I_n$$

$$I_n = -6.24 - 4.24j \quad V_{oc} = 6.24j - 4.42$$

$$V_{oc}/I_n = R_n \quad R_n = -j$$

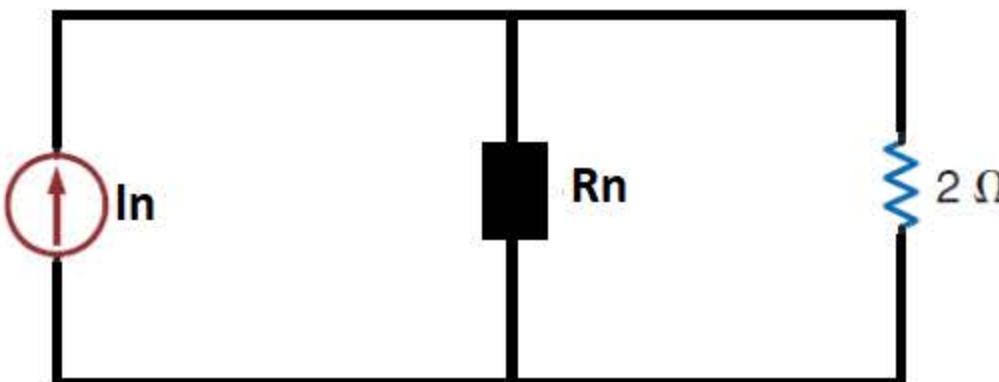

2Ω üzerinden geçen akım = I_o

$$I_o = I_n \times (R_n / R_n + 2)$$

$$I_o = (-6.24 - 4.24j) \times (-j / 2-j), \quad (-6.24 - 4.24j) \times (0.2 - 0.4j)$$

$$I_o = -2.94 + 1.64j$$


$$I_o = 3.366 \angle -29.153$$

8.142

$$16 \cos(377t + 45^\circ) = 16 \angle 45$$

$$2\text{mH} = j \times 377 \times 2 \times 10^{-3}$$

$$Z_L = 0.384j$$

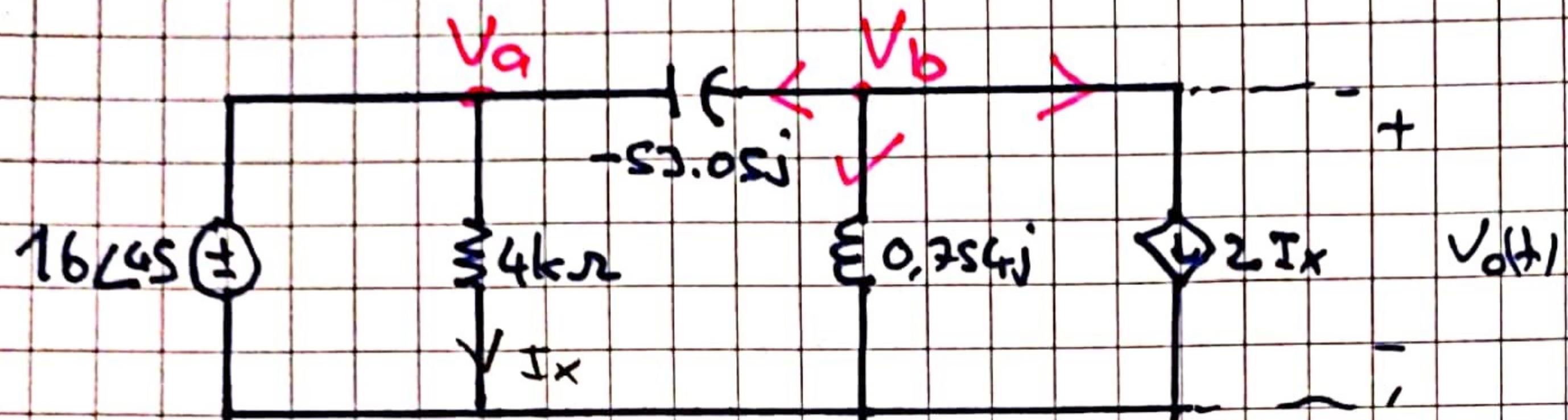

$$I_x = \frac{16 \angle 45}{4 \times 10^3} = \frac{11.31 + 11.31j}{4 \times 10^3} = 2.8225 \times 10^{-3} (1+j)$$

$$\frac{(V_b - 11.31 - 11.31j)}{-53.05j} + \frac{V_b}{0.384j} - 2 \times (2.8225 \times 10^{-3} (1+j)) = 0$$

(-20) Yalnızca 30 koltuk $30 \times 0.384 = -53.05$

$$V_b - 11.31 - 11.31j - 30V_b = 106k(2.8225 \times 10^{-3} (1+j))$$

$$-69V_b = 0.29 + 0.29j + 11.31 + 11.31j$$

$$-11.6 - 11.6j = 69V_b$$

$$-0.16 - 0.16j = V_b = V_o, \quad V_o = 0.22 \angle 45$$

$$\boxed{V_o(t) = 0.22 \cos(377t + 45)}$$

142 Find $v_o(t)$ in the network in Fig. P8.142.

